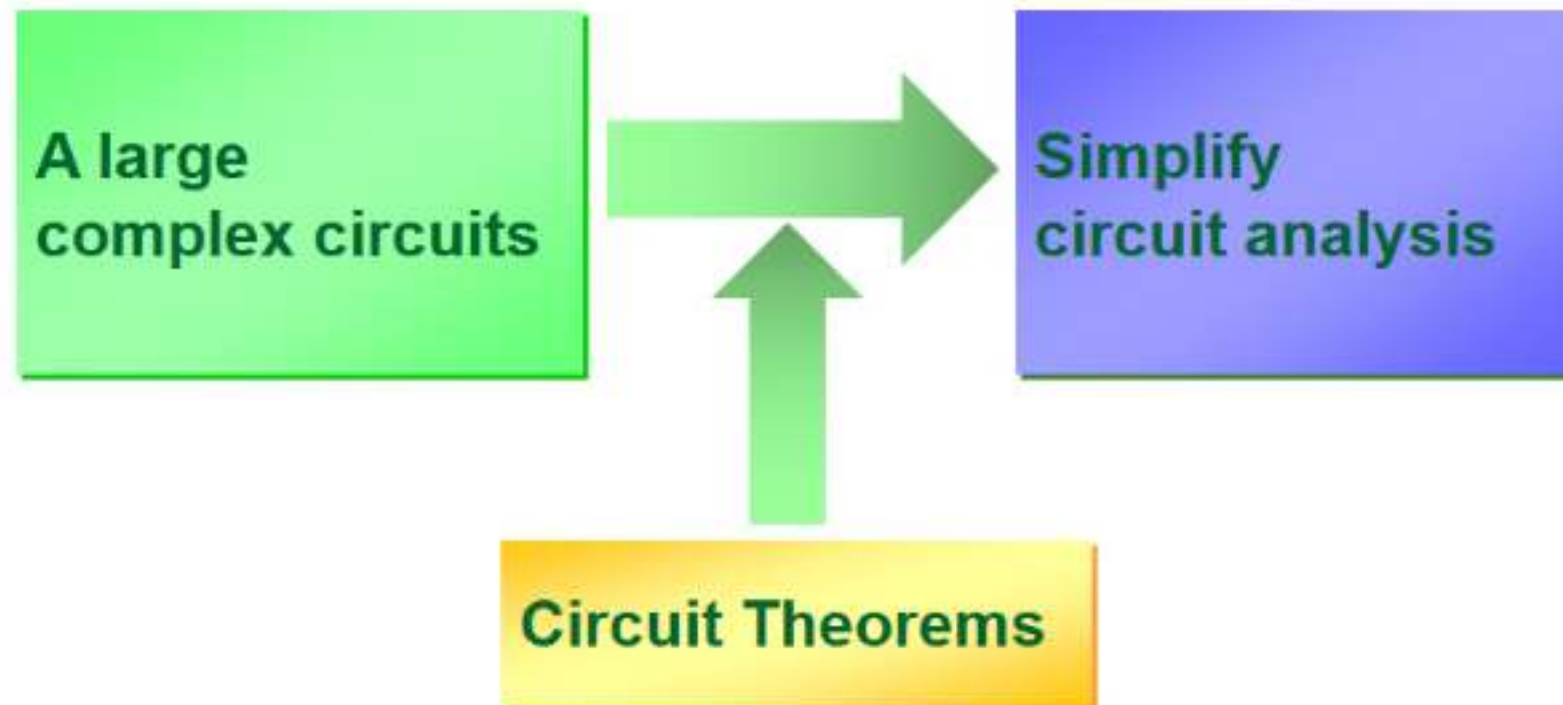


UNIT-1

CIRCUIT THEOREMS

By
Ch. V. Krishna Reddy
EEE,CBIT

Introduction



- Thevenin's theorem
- Circuit linearity
- source transformation
- Norton theorem
- Superposition
- max. power transfer

Topics to be Discussed



- Superposition Theorem.
- Thevenin's Theorem.
- Norton's Theorem.

Superposition Theorem


- The response (current or voltage) in a linear network at any point due to multiple sources (current and/or emf) can be calculated by summing the effects of each source considered separately,
- Turn off, killed, inactive source:
 - independent voltage source: 0 V (short circuit)
 - independent current source: 0 A (open circuit)
- Dependent sources are left intact.

Superposition Theorem


How to “Turning off” sources

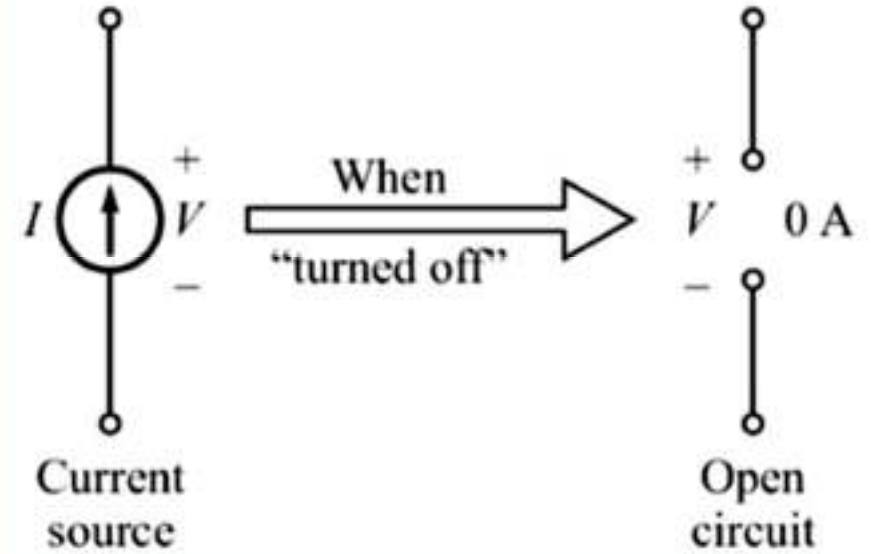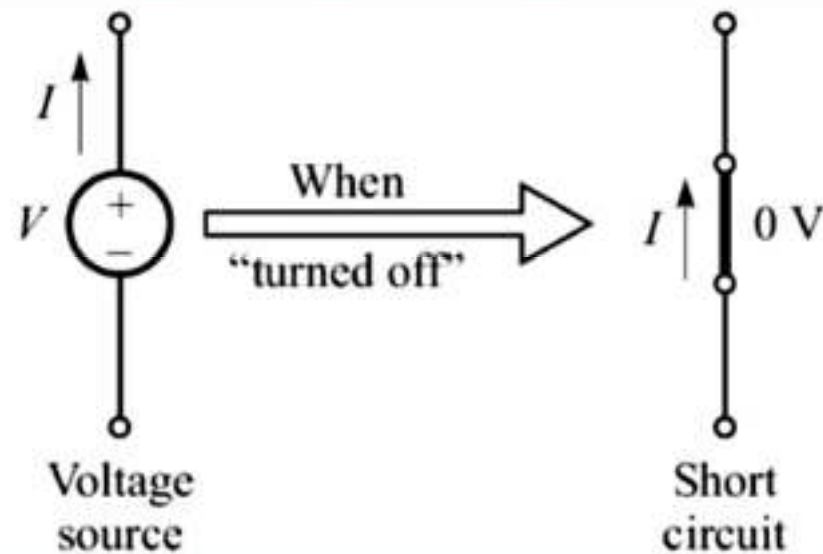

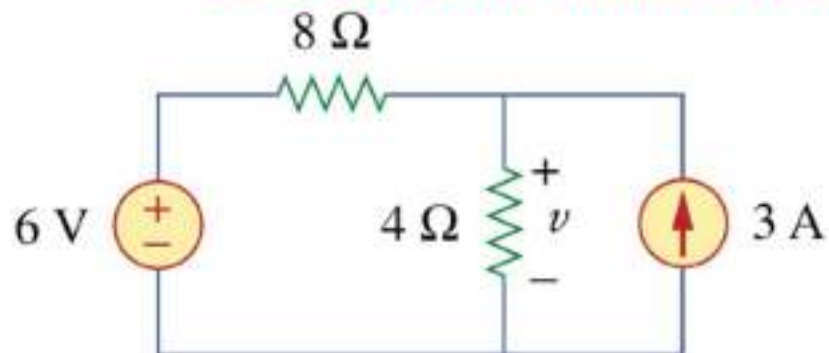Ex:1 Use superposition theorem to find 'v' in the circuit in Fig.




(i) consider voltage source of 6V alone

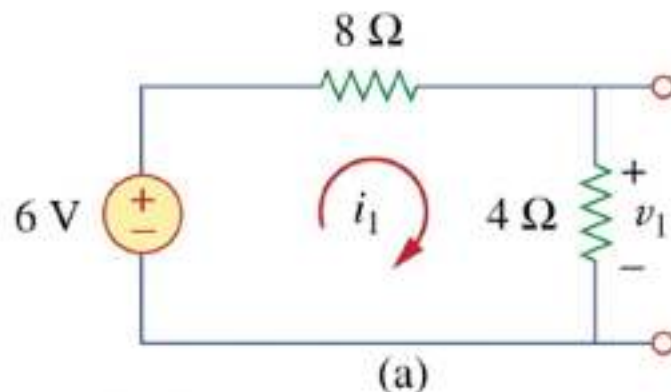

Apply VDR to get V_1

$$V_1 = \frac{4}{4+8}(6) = 2V$$

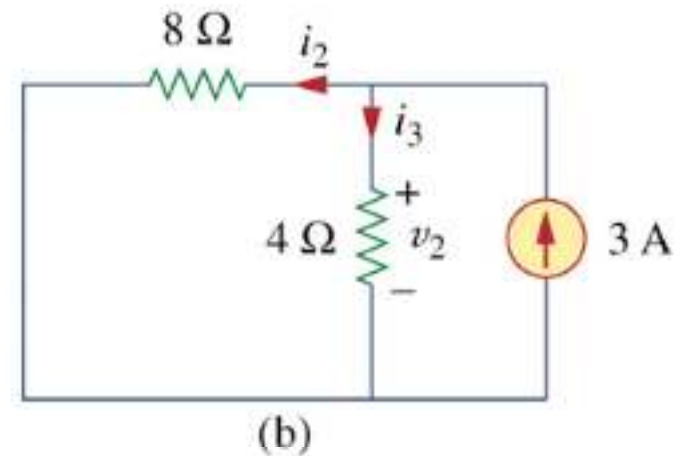(ii) consider current source of 3 A alone



Apply CDR to get i_3


$$i_3 = \frac{8}{4+8}(3) = 2A$$

Hence $v_2 = 4i_3 = 8V$

Finally find


$$v = v_1 + v_2 = 2 + 8 = 10V$$

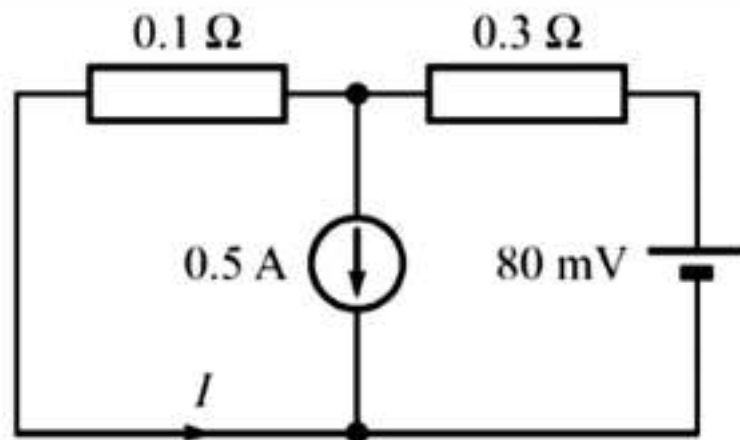Ex: 2 Find the current I in the circuit given, using superposition theorem.



$$I_1 = -\frac{0.5 \times 0.3}{0.1 + 0.3} = \frac{-0.15}{0.4} = -\mathbf{0.375\text{ A}}$$

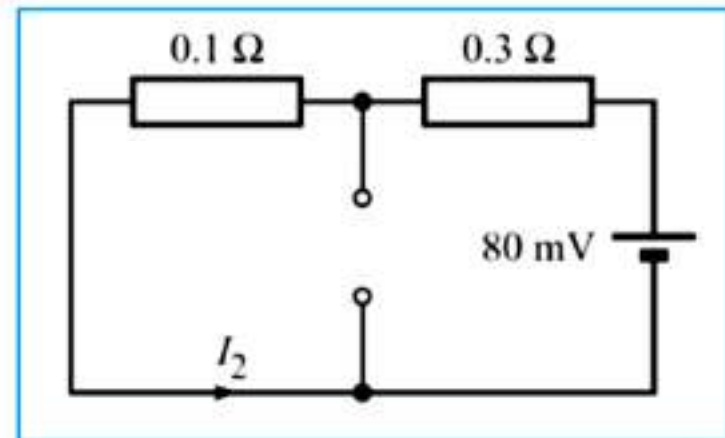
(ii) Next, consider the voltage source of 80mV alone,




$$I_2 = \frac{80 \times 10^{-3}}{0.1 + 0.3} = \mathbf{0.2\text{ A}}$$

$$\therefore I = I_1 + I_2 = -\mathbf{0.175\text{ A}}$$

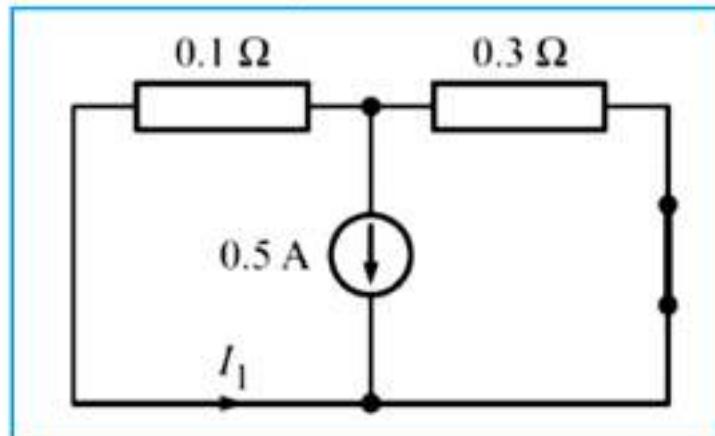
(i) First, consider the current source of 0.5 A alone,



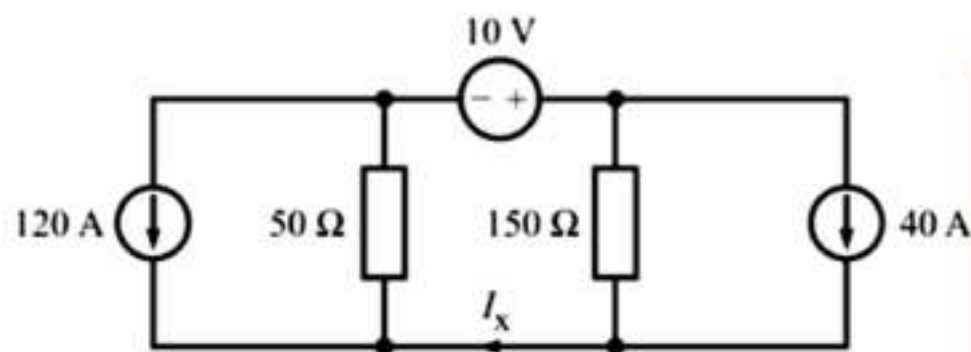Ex:3 Using superposition theorem, find current i_x in the network given.




(i) Consider 10-V source alone

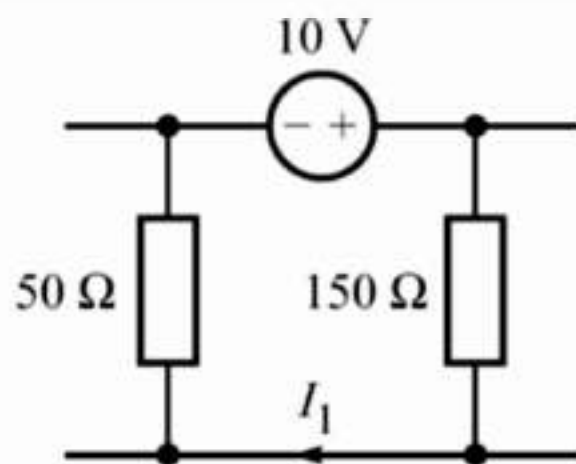


$$i_1 = \frac{10}{50 + 150} = 0.05 \text{ A}$$

(ii) Consider 40-A source alone

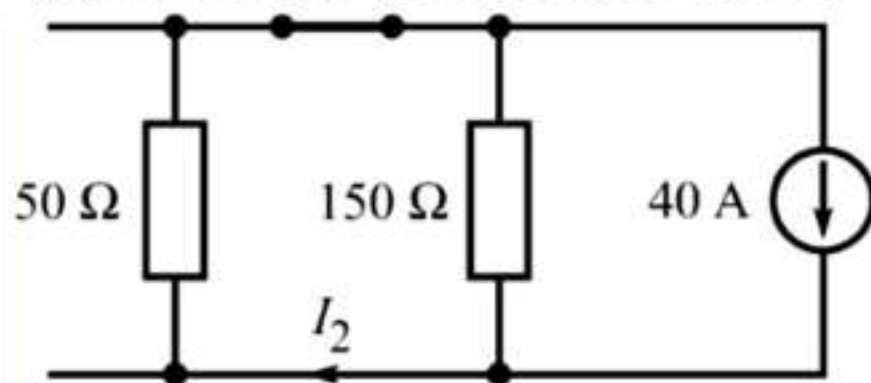

$$i_2 = 40 \times \frac{150}{50 + 150} = 30 \text{ A}$$

(iii) Consider 120-A source alone

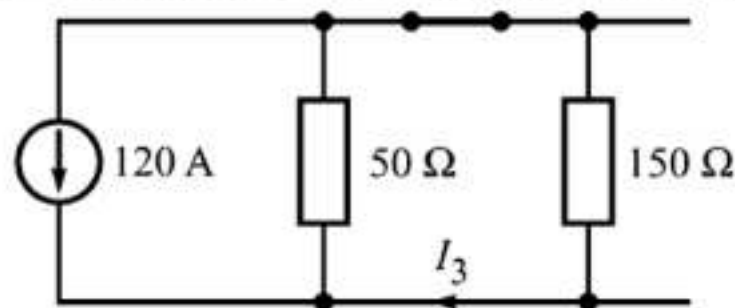


$$i_3 = -120 \times \frac{50}{50 + 150} = -30 \text{ A}$$


Ex:3 Using superposition theorem, find current i_x in the network given. In the end, the total response due to all the sources working together is

$$\begin{aligned} i_x &= i_1 + i_2 + i_3 \\ &= 0.05 + 30 - 30 \\ &= \mathbf{0.05 \text{ A}} \end{aligned}$$

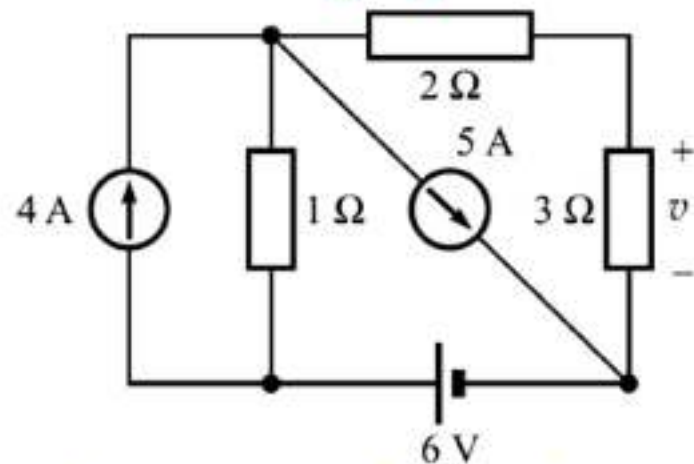Ex:4 Find voltage v across 3- Ω resistor by applying the principle of superposition.



(i) response due to 4-A source alone

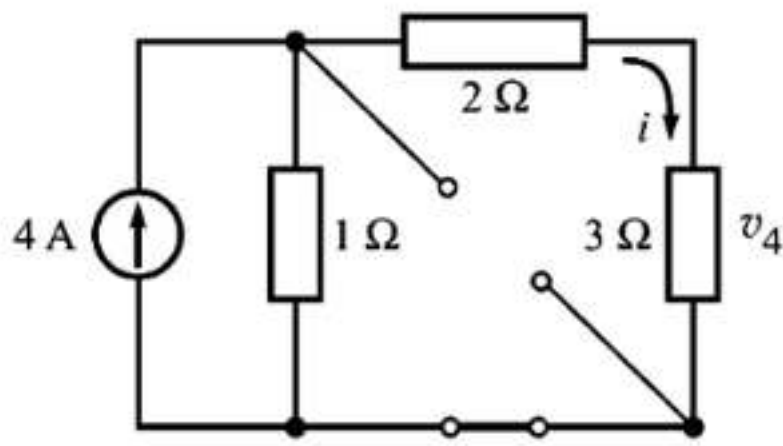


Using CDR

$$i = 4 \times \frac{1}{1 + (2 + 3)} = \frac{2}{3} \text{ A}$$

$$\begin{aligned} \therefore v_4 &= i \times R \\ &= \left(\frac{2}{3} \text{ A}\right) \times (3 \Omega) \\ &= 2.0 \text{ V} \end{aligned}$$

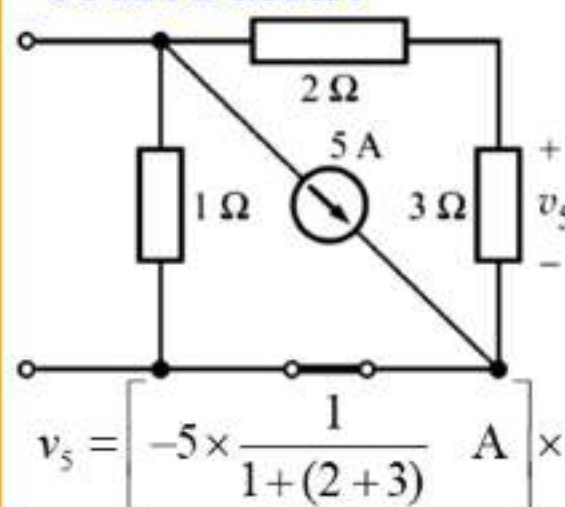(ii) Next, the response due to 5-A source alone




Using CDR, voltage v_5 across 3- Ω

$$v_5 = \left[-5 \times \frac{1}{1 + (2 + 3)} \text{ A} \right] \times (3 \Omega) = -2.5 \text{ V}$$

Ex:4 Find voltage v across $3\text{-}\Omega$ resistor by applying the principle of superposition.

(iii) response due to 6-V source alone

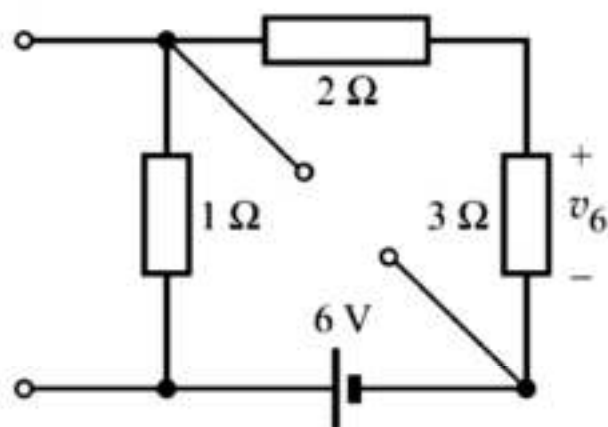


By voltage divider,

$$v_6 = 6 \times \frac{3}{1+2+3} = 3.0 \text{ V}$$

$$\therefore v = +v_4 + v_5 + v_6 = +2.0 - 2.5 + 3.0 = +\mathbf{2.5 \text{ V}}$$

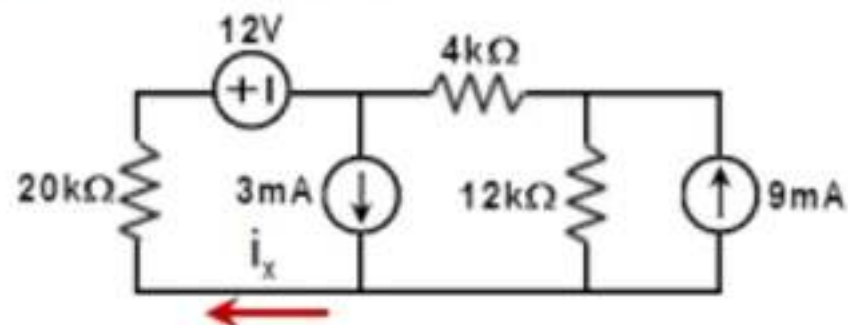
Ex: 5 Use superposition to find the current i_x through the $20\text{ k}\Omega$ resistor ?



Superposition states that to calculate the current $i_{20k\Omega}$, this current is the sum of all of the individual currents produced by the 12V, 3mA and 9mA-sources:


$$i_{20k} = i_{12V} + i_{3mA} + i_{9mA} \equiv i_1 + i_2 + i_3$$

(i) Response of the 12V-source

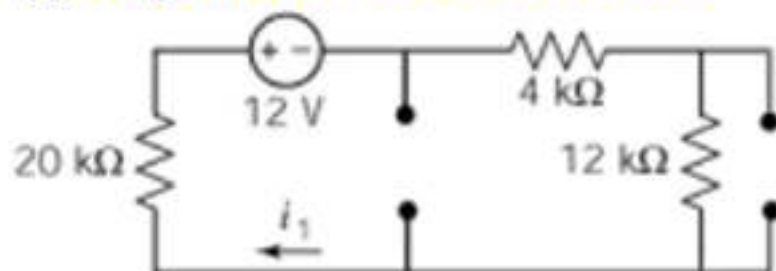


$$36 \cdot i_1 = -12 \longrightarrow i_1 = -\frac{1}{3} \text{ mA}$$

(ii) Response of the 3mA-source

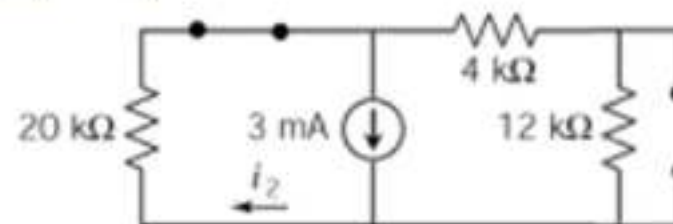

$$i_2 = \frac{16}{16+20}(3\text{mA}) = \boxed{\frac{4}{3} \text{ mA} = i_2}$$



(iii) Response of the 9mA-source

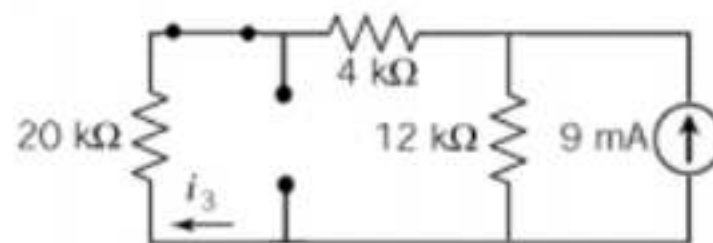


$$i_3 = \frac{12}{12+24}(9\text{A}) = \boxed{-3 \text{ mA} = i_3}$$

$$i_{20k\Omega} = i_1 + i_2 + i_3$$

$$= -\frac{1}{3} + \frac{4}{3} - 3 = \boxed{-2 \text{ mA} = i_{20k\Omega}}$$

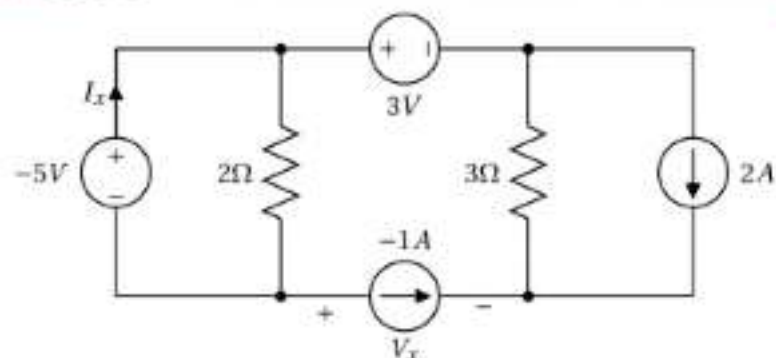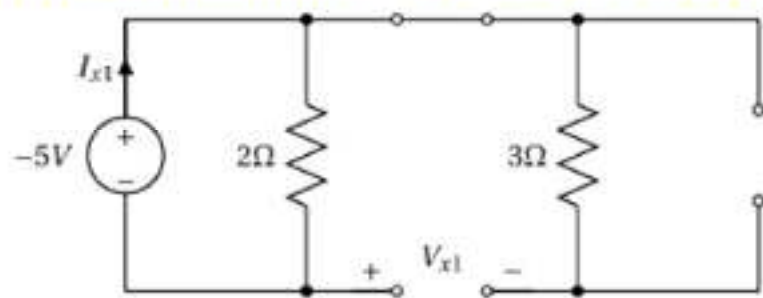Ex: 6 Determine V_x and I_x using the superposition method**(i) Contribution of -5V voltage source:**Using KVL, $-(-5V) + V_{3\Omega} - V_{x1} = 0$


$$V_{x1} = -(-5V) = 5V$$

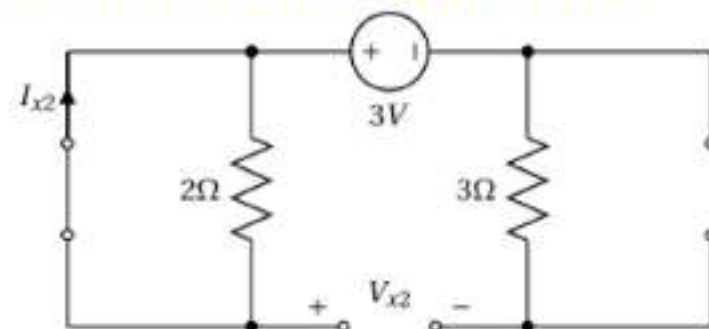(ii) Contribution of the 3V voltage source:

Using KVL

$$-(3V) + V_{2\Omega} + V_{x2} + V_{3\Omega} = 0$$


$$V_{x2} = 3V$$

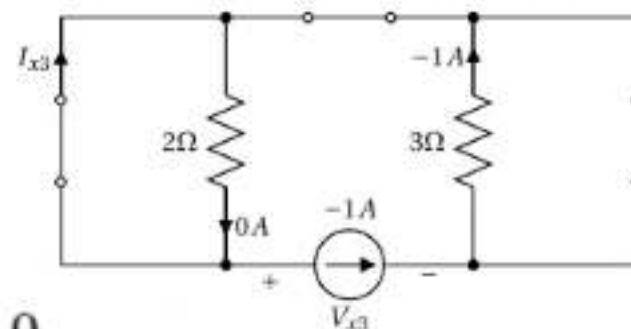(iii) Contribution of the -1A current source:

Using KVL

$$V_{x3} + V_{3\Omega} = 0$$

$$V_{x3} + (-1A) \times (3\Omega) = 0 \quad V_{x3} = 3V$$

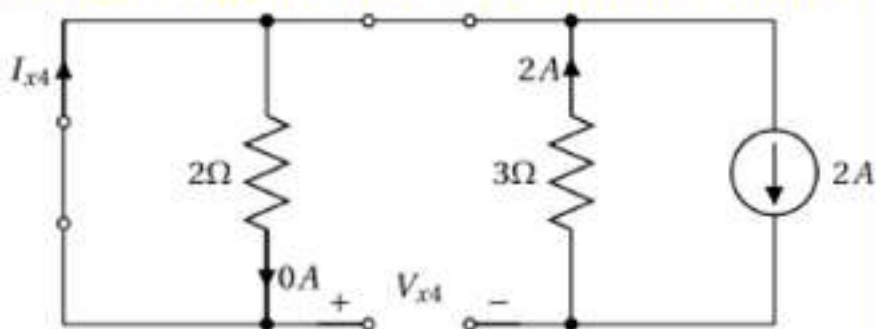Ex: 6 Determine V_x and I_x using the superposition method**(iv) Contribution of the 2A current source:**

Using KVL

$$V_{x4} + V_{3\Omega} = 0$$

$$V_{x4} + (2A) \times (3\Omega) = 0$$

$$V_{x4} = -6V$$

V. Adding up the individual contributions algebraically:

$$V_x = V_{x1} + V_{x2} + V_{x3} + V_{x4}$$



$$= 5V + 3V + 3V - 6V$$

$$V_x = 5V$$


$$I_x = I_{x1} + I_{x2} + I_{x3} + I_{x4}$$

$$= -2.5A + 1A + 0A - 0A$$


$$I_x = -1.5A$$

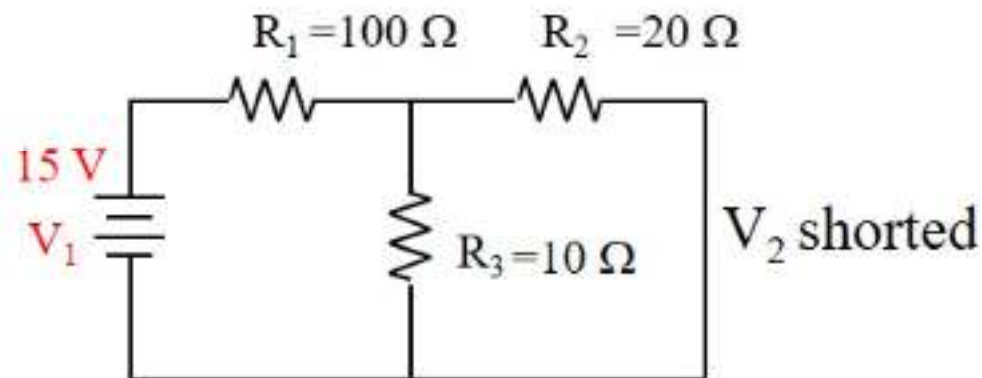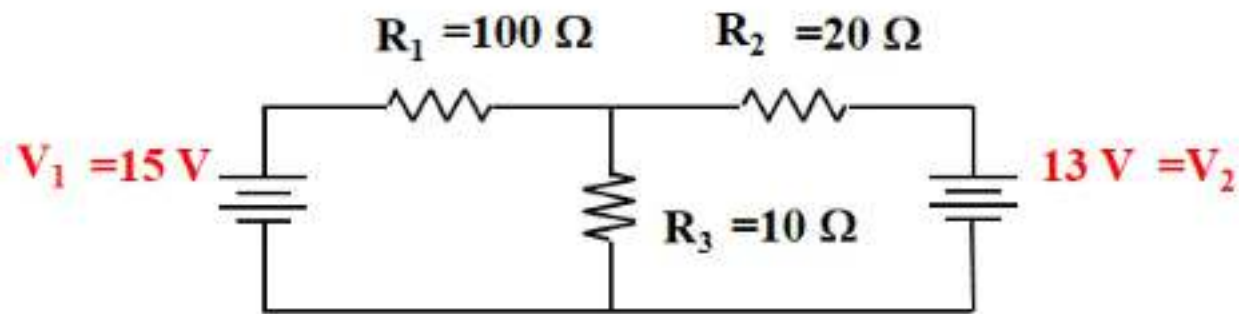Ex: 7 Using superposition theorem find current in R_3 

$$R_{EQ} = 106.7\ \Omega, I_T = 0.141\text{ A and } I_{R_3} = 0.094\text{ A}$$

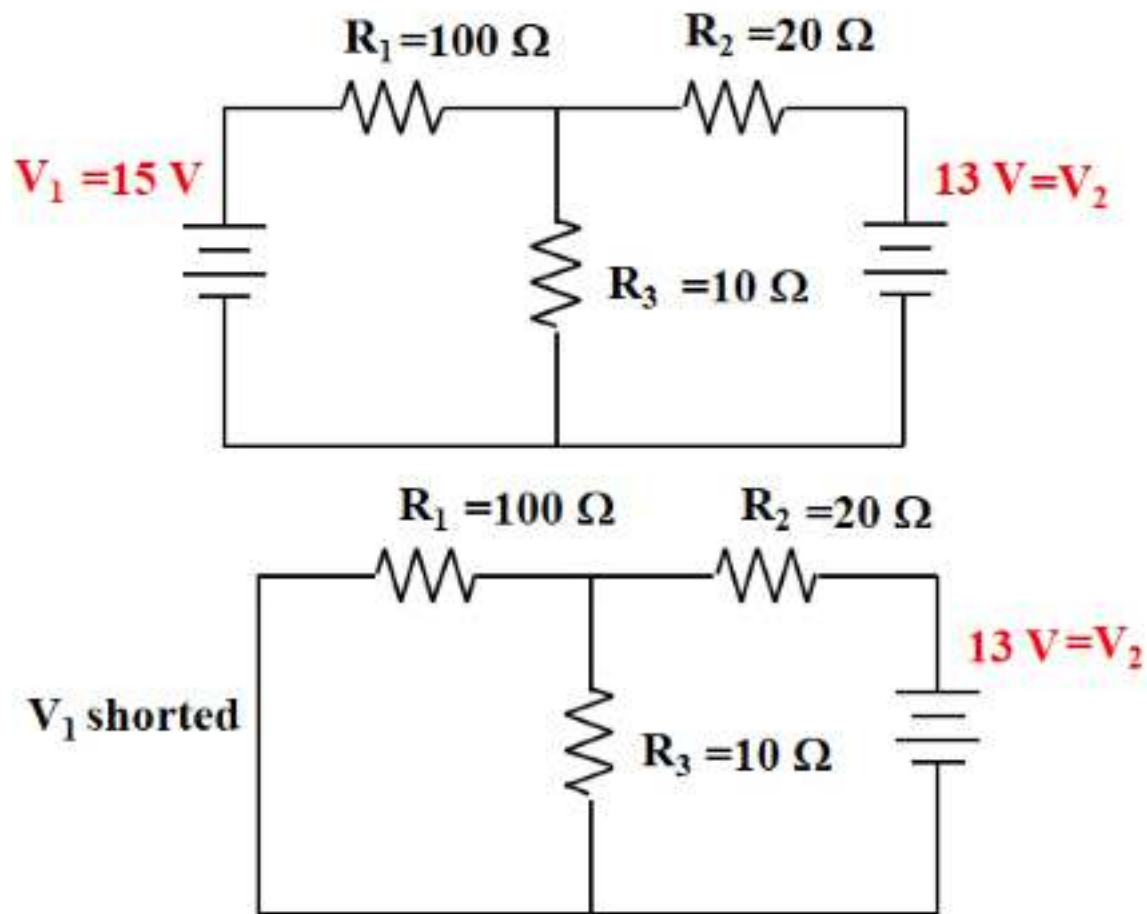Ex: 7 Using superposition theorem find current in R_3 

$$R_{EQ} = 29.09\ \Omega, I_T = 0.447\text{ A and } I_{R_3} = 0.406\text{ A}$$

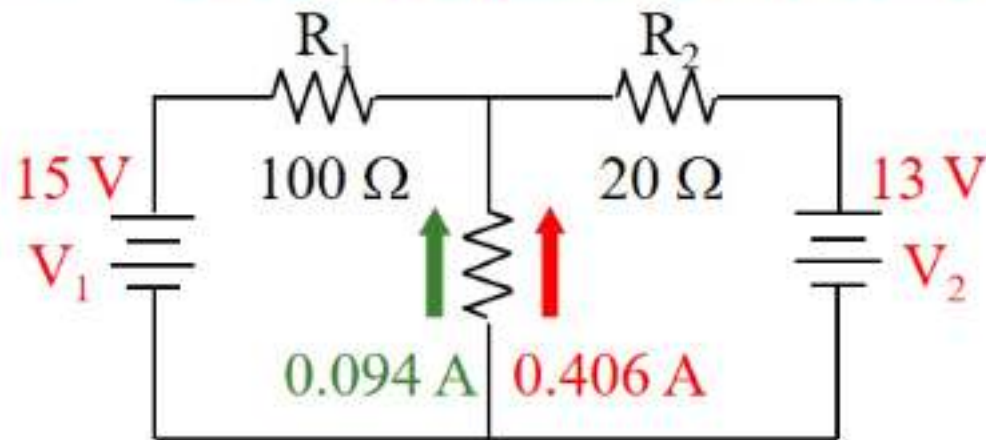Ex: 7 Using superposition theorem find current in R_3 

With V_2 shorted

$$R_{\text{EQ}} = 106.7\ \Omega, I_T = 0.141\text{ A and } I_{R_3} = 0.094\text{ A}$$

With V_1 shorted

$$R_{\text{EQ}} = 29.09\ \Omega, I_T = 0.447\text{ A and } I_{R_3} = 0.406\text{ A}$$

Adding the currents gives $I_{R_3} = 0.5\text{ A}$

Thevenin's Theorem

- **Statement:** It states that a linear two-terminal circuit (Fig. a) composed of passive and active elements can be replaced by an equivalent circuit (Fig. b) consisting of a voltage source V_{TH} in series with a resistor R_{TH} ,
- where
- V_{TH} is the open-circuit voltage at the load terminals.
- R_{TH} is the input or equivalent resistance at the terminals when the independent sources are turned off.

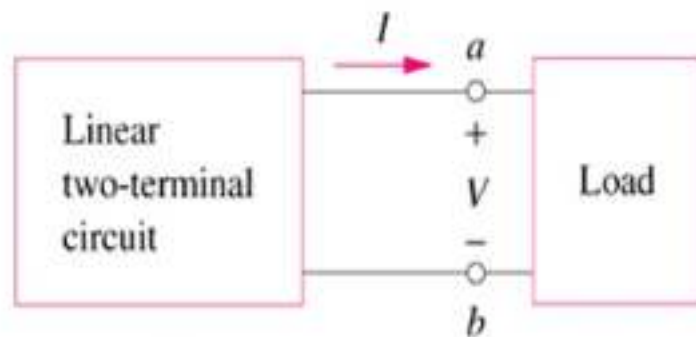


Fig. a

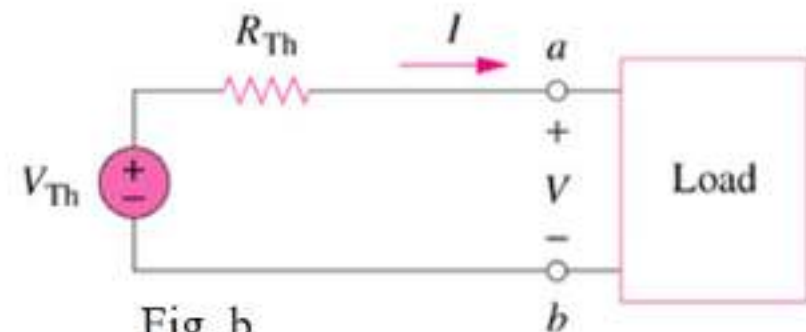



Fig. b

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

Thevenin's Theorem


■ Calculation of V_{Th}

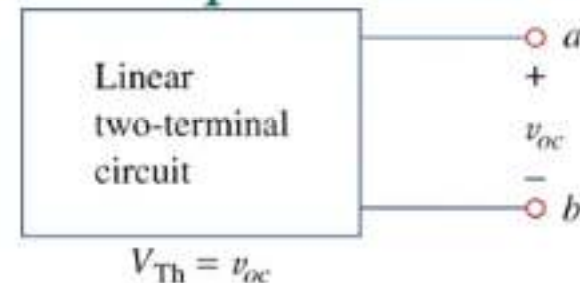The voltage V_{Th} is equal to the potential difference between the two terminals 'ab' caused by the active network with **no external resistance (load)** connected to these terminals. Hence, it is called **open-circuit voltage**, V_{oc} .




■ Calculation of R_{Th}

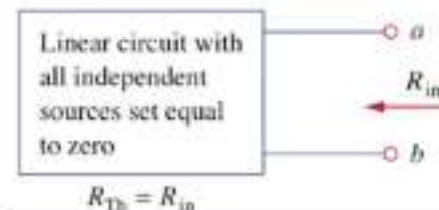The series resistance R_{Th} is the equivalent resistance looking back into the network at the terminals 'ab' with **all the sources** within the network made **inactive**, or dead.




Thevenin's Theorem

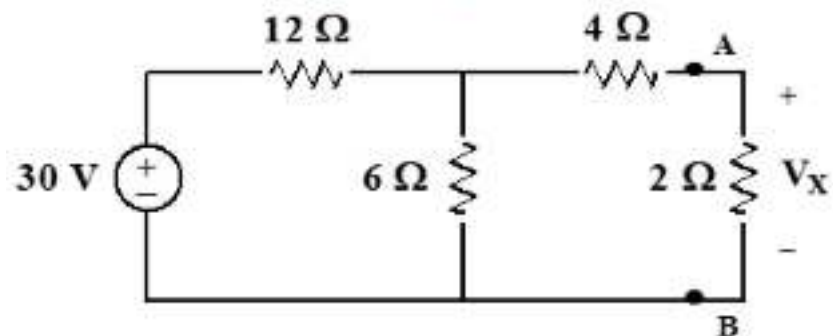EX:1 Find V_X using Thevenin theorem for the circuit shown in Fig.




(i) Find V_{th}

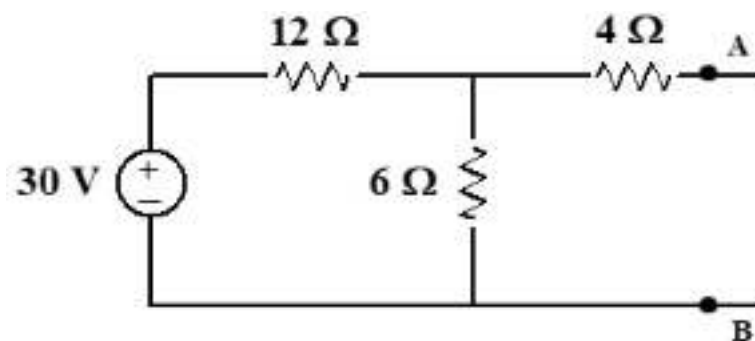

$$V_{AB} = \frac{(30)(6)}{6+12} = 10V$$


10

(ii) Find R_{th}

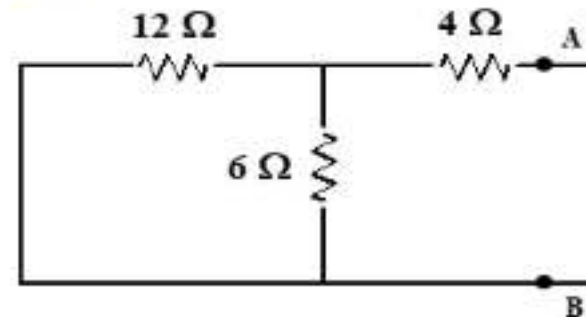

$$R_{TH} = 12 || 6 + 4 = 8 \Omega$$


(iii) Thevenin equivalent circuit

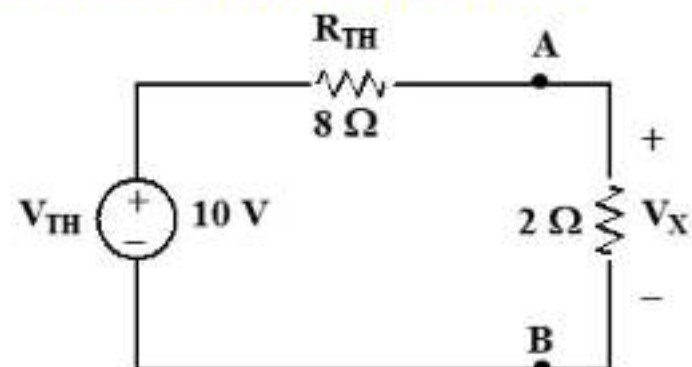

$$V_X = \frac{(10)(2)}{2+8} = 2V$$


Thevenin's Theorem

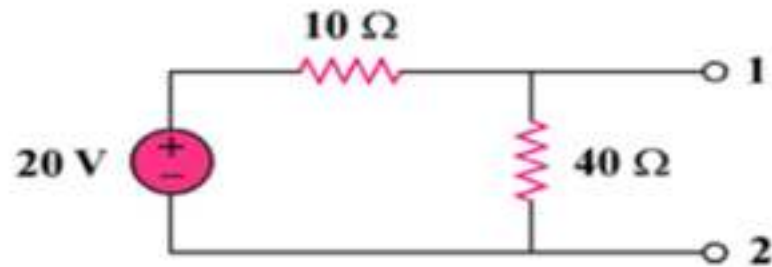EX:2 Find R_{th} and V_{th} at terminals 1-2 of the given circuit




Solution:

(i) Find R_{th}

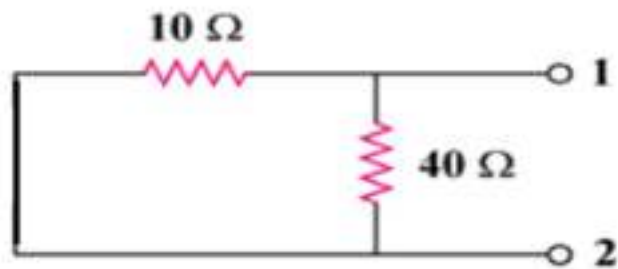

$$R_{Th} = 10 \parallel 40 = 400/50 = \underline{\underline{8 \text{ ohms}}}$$

(ii) Find V_{th}

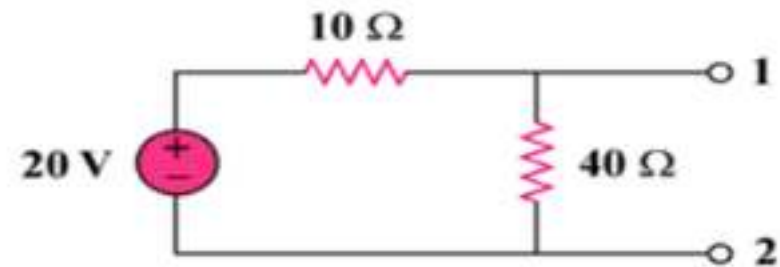


Use VDR

$$V_{Th} = (40/(40 + 10))20 = \underline{\underline{16 \text{ V}}}$$


Thevenin's Theorem

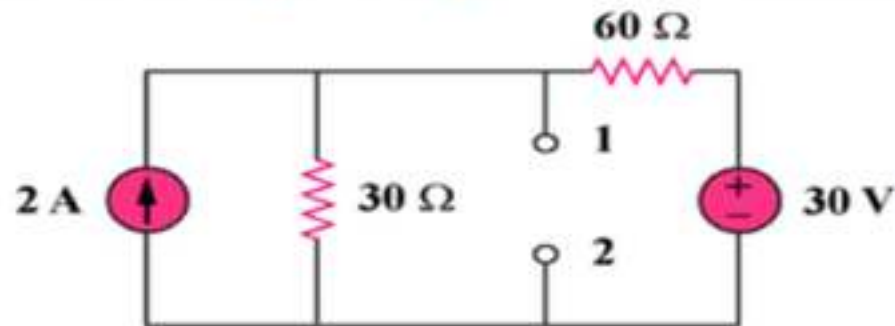EX:3 Find R_{th} and V_{th} at terminals 1-2 of the given circuit




Solution:

(i) Find R_{th}

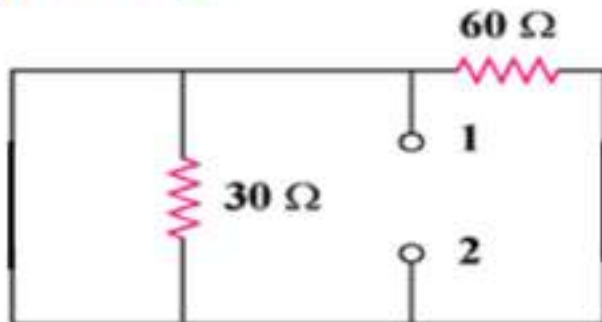

$$R_{Th} = 30 \parallel 60 = 1800/90 = \underline{\underline{20 \text{ ohms}}}$$

(ii) Find V_{th}

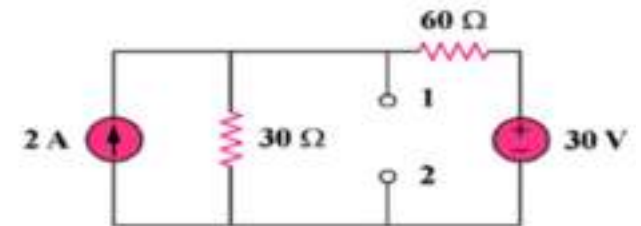



$$2 + (30 - v_1)/60 = v_1/30, \text{ and } v_1 = V_{Th}$$

$$120 + 30 - v_1 = 2v_1, \text{ or } v_1 = 50 \text{ V}$$


$$V_{Th} = \underline{\underline{50 \text{ V}}}$$

Thevenin's Theorem

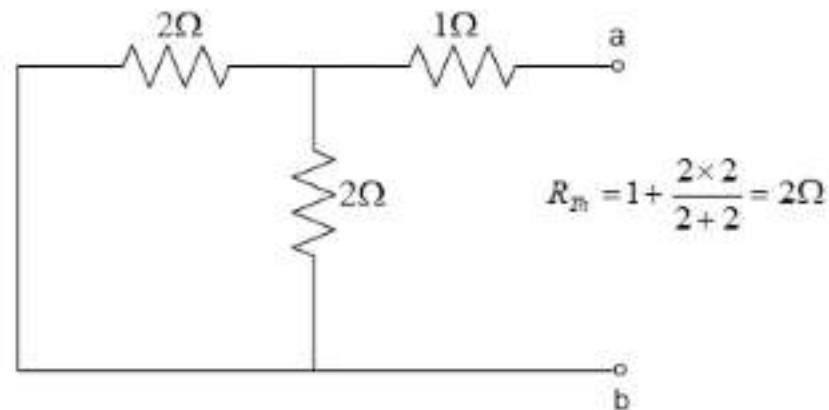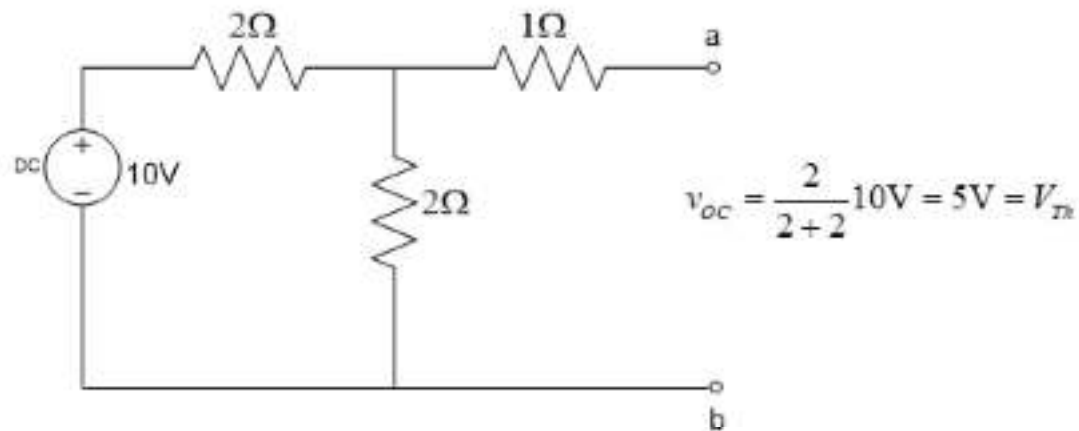EX:4 Find the Thevenin equivalent circuit of the circuit shown in Fig.






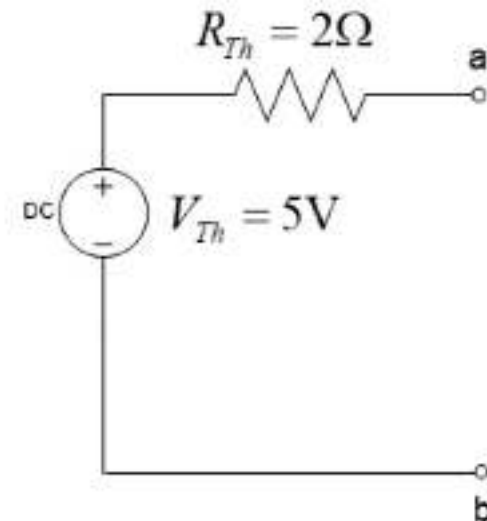
$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{5}{2.5} = 2\Omega$$



Thevenin's Theorem

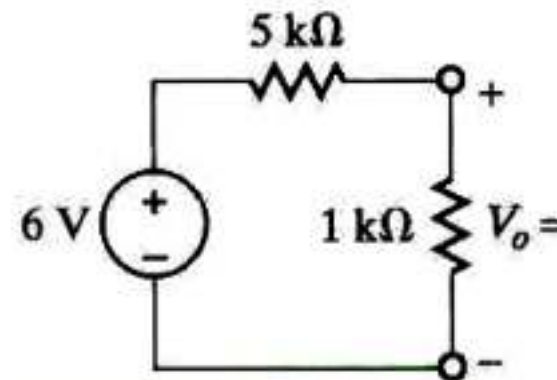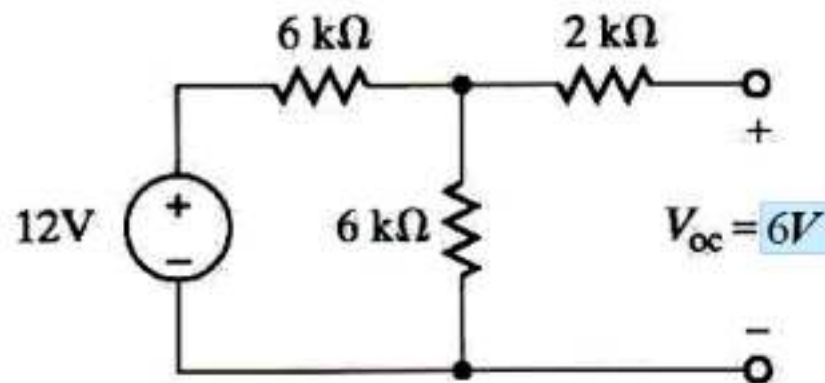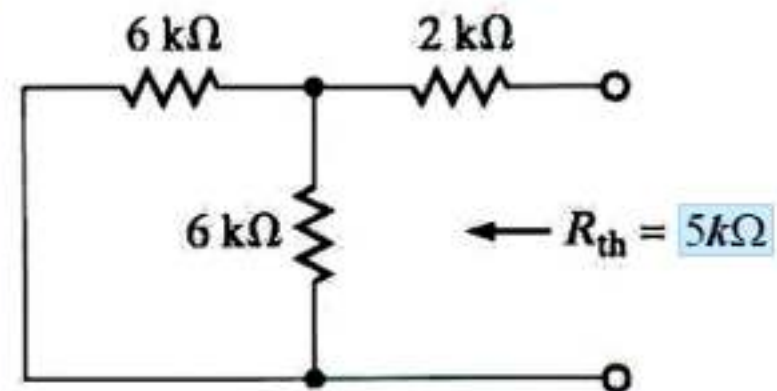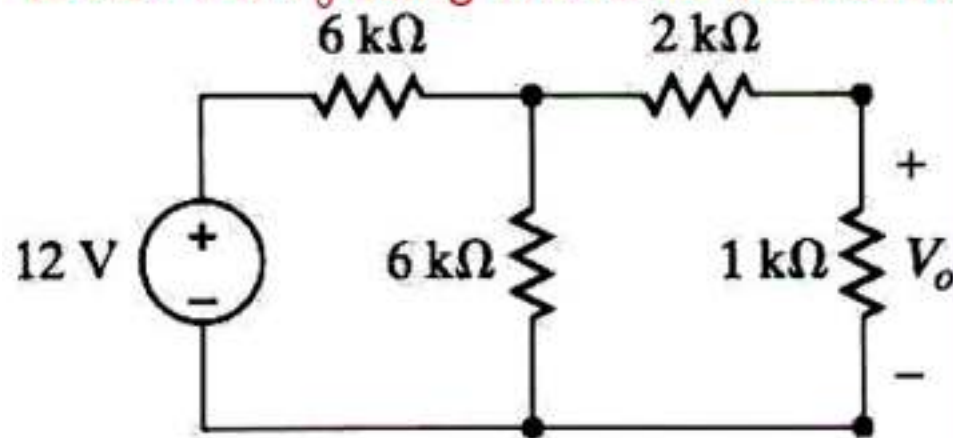
EX:5 Find V_o using Thevenin theorem for the circuit shown in Fig.



$$V_o = \frac{1k}{1k + 5k} (6V) = 1[V]$$


Thevenin's Theorem

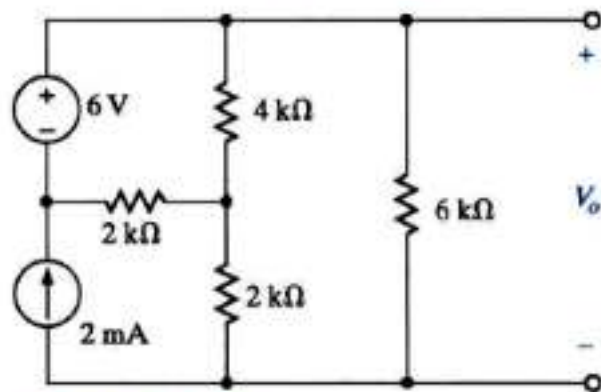EX:6 Find V_o using Thevenin theorem for the circuit shown in Fig.



Solution:

(i) Find R_{th}

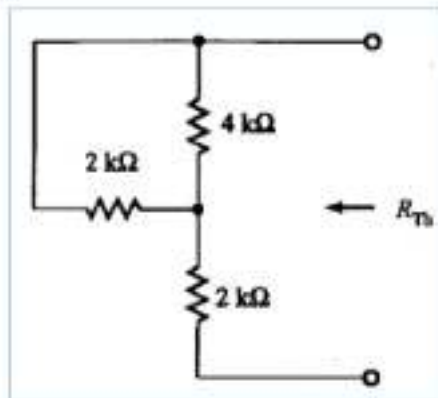

(ii) Find V_{th}


Loop Analysis

$$I_2 = 2mA$$


$$-6V + 4kI_1 + 2k(I_1 - I_2) = 0$$

$$I_1 = \frac{6 + 2I_2}{6} mA = \frac{5}{3} mA$$
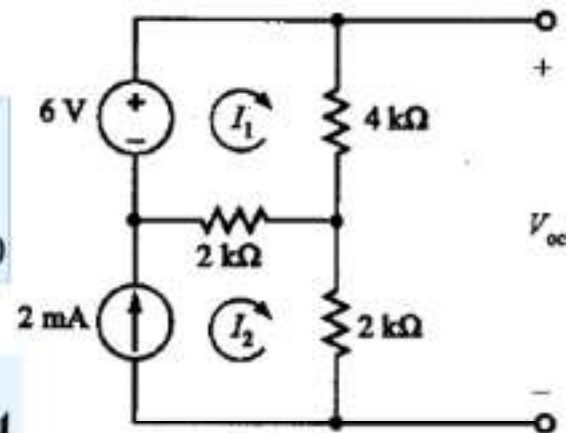
$$V_{oc} = 4k * I_1 + 2k * I_2 = 20/3 + 4V = 32/3[V]$$




(iii) Thevenin equivalent circuit

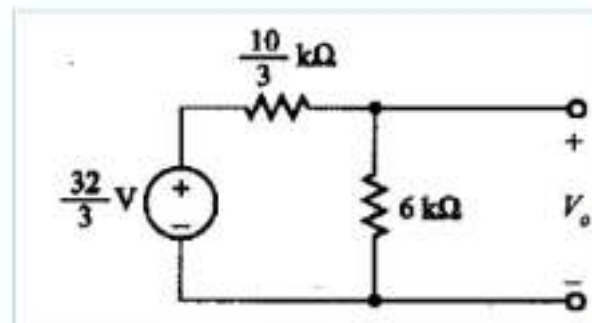


Thevenin's Theorem

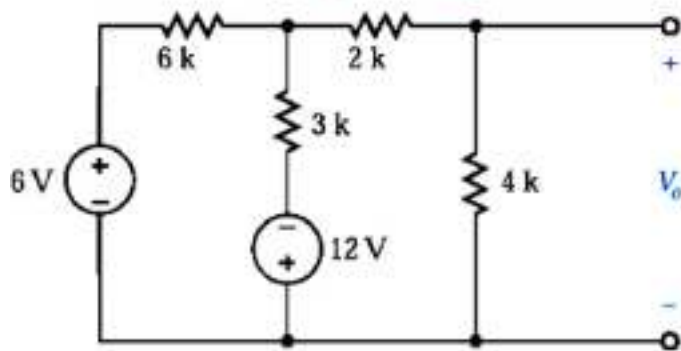EX:7 Find V_o using Thevenin theorem for the circuit shown in Fig.



Solution:


(i) Find V_{th}

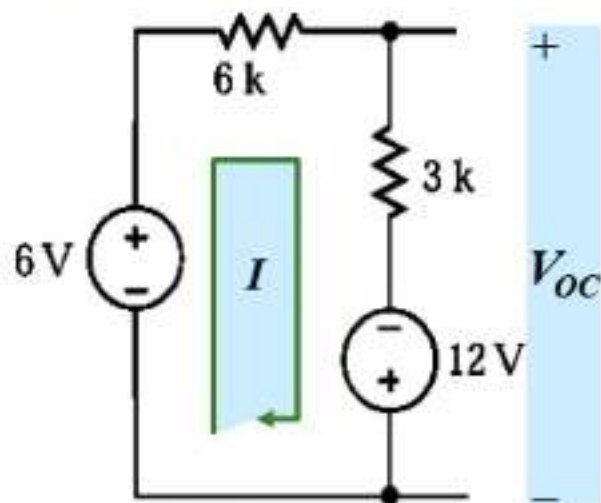


$$9kI = 18[V] \Rightarrow I = 2mA$$

$$V_{oc} = 3kI - 12 = -6[V]$$

(ii) Find R_{th}

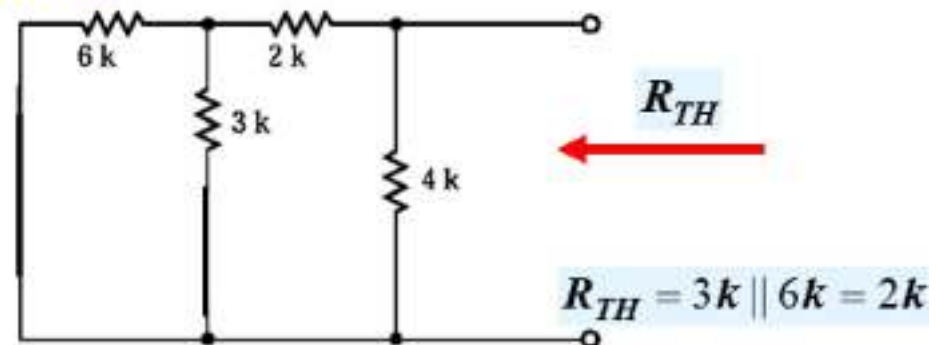

(iii) Thevenin equivalent circuit

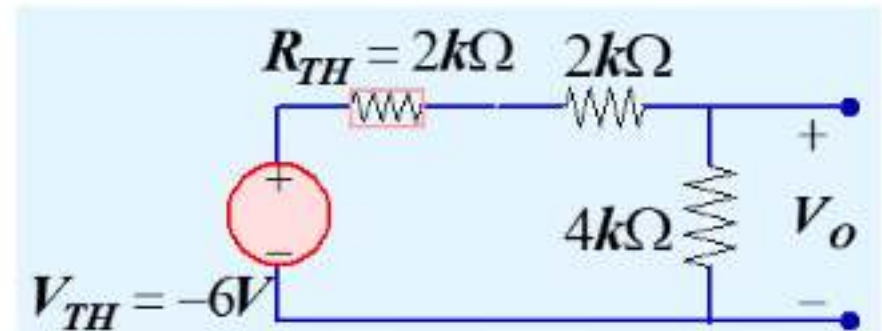


$$V_o = \frac{4}{4+4}(-6V) = -3[V]$$




Thevenin's Theorem

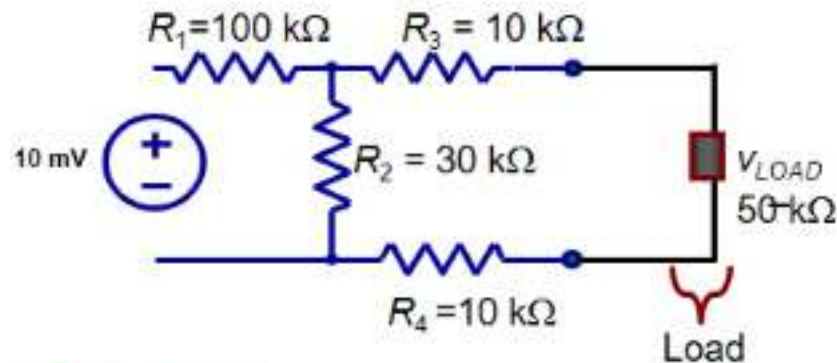EX:8 Find voltage across 50 K Ω using Thevenin theorem in the given circuit




Solution:

(i) Find R_{th}

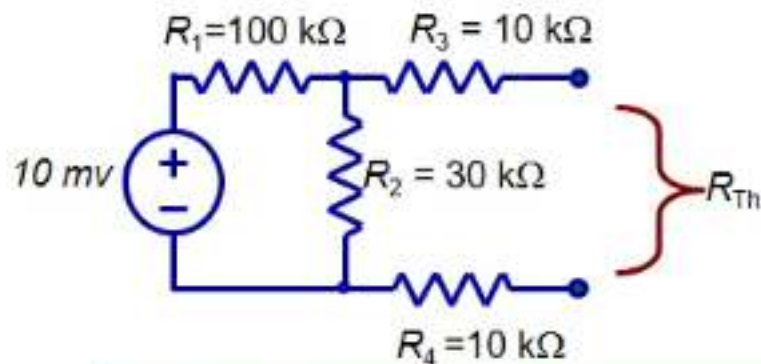


$$\begin{aligned} R_{Th} &= R_3 + R_1 \parallel R_4 \\ &= 10 \text{ k}\Omega + 23 \text{ k}\Omega + 10 \text{ k}\Omega \\ &= 43 \text{ k}\Omega \end{aligned}$$

(ii) Find V_{th}

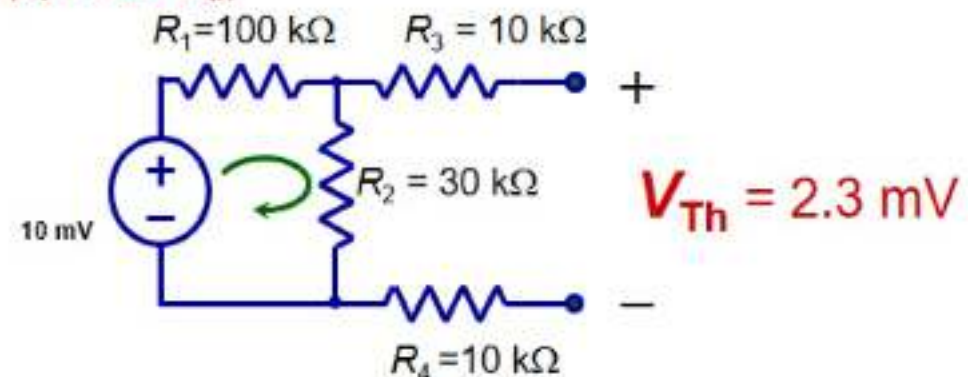

- From KVL around the inner loop
 $v_2 = 10 * R_2 / (R_1 + R_2) = 2.3 \text{ mV}$


(iii) Thevenin equivalent circuit

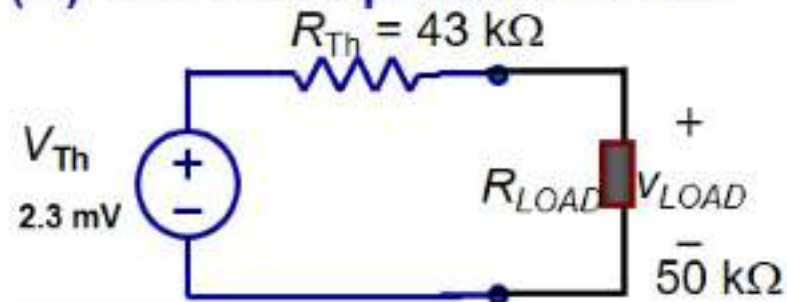


$$\begin{aligned} V_{LOAD} &= V_{Th} (R_{LOAD} / (R_{LOAD} + R_{Th})) = 2.3 \text{ mV} \times (50 \text{ k}\Omega) / (93 \text{ k}\Omega) \\ &= \mathbf{0.54 \text{ mV}} \end{aligned}$$

Thevenin's Theorem

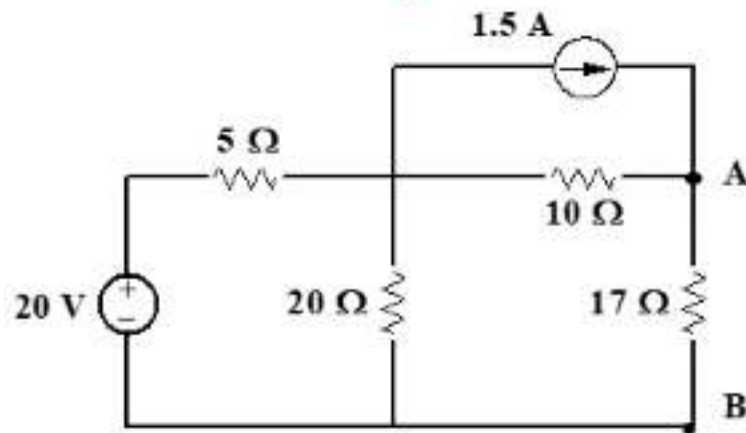EX:9 Find voltage across 17Ω using Thevenin theorem in the given circuit




(i) Find V_{th}

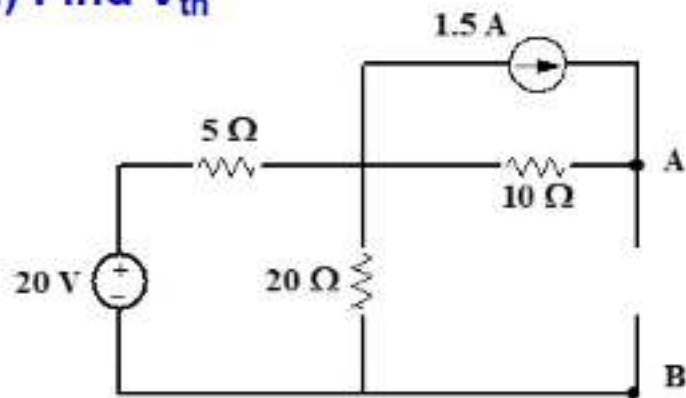

$$V_{OS} = V_{AB} = V_{TH} = (1.5)(10) + \frac{20(20)}{(20+5)}$$


$$\therefore V_{TH} = 31V$$

(ii) Find R_{th}

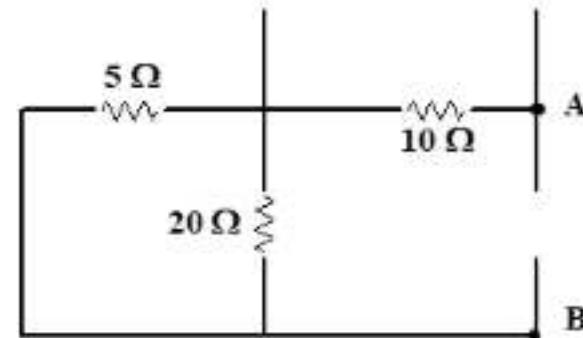

$$R_{TH} = 10 + \frac{5(20)}{(5+20)} = 14\Omega$$


(iii) Thevenin equivalent circuit

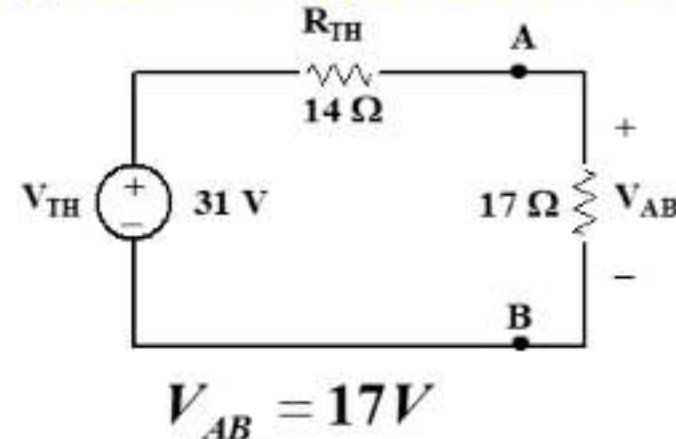


$$V_{AB} = 17V$$

Thevenin's Theorem

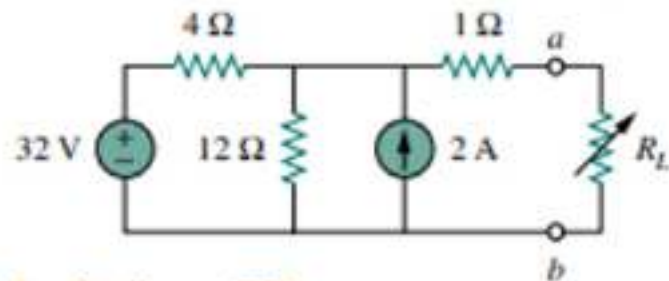EX:10 Find the Thevenin equivalent circuit of the circuit shown in Fig. Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$



Calculation of V_{Th}

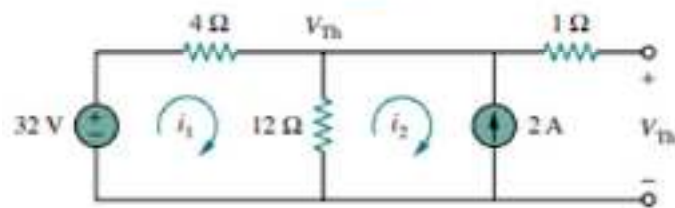

Using mesh analysis

$$-32 + 4i_1 + 12(i_1 - i_2) = 0,$$

$$i_2 = -2 \text{ A}$$

Solving for i_1 , we get $i_1 = 0.5 \text{ A}$. Thus,

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$


Using Nodal analysis

$$\frac{32 - V_{Th}}{4} + 2 = \frac{V_{Th}}{12}$$

$$96 - 3V_{Th} + 24 = V_{Th}$$

$$V_{Th} = 30 \text{ V}$$

Resultant circuit

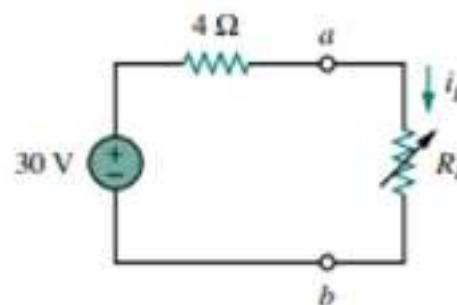

When $R_L = 6$,

When $R_L = 16$,

When $R_L = 36$,


$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

$$I_L = \frac{30}{10} = 3 \text{ A}$$

$$I_L = \frac{30}{20} = 1.5 \text{ A}$$



$$I_L = \frac{30}{40} = 0.75 \text{ A}$$

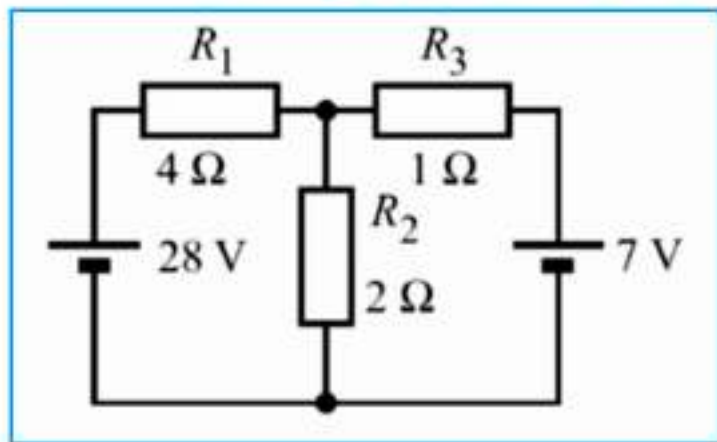Ex: 11 Using Thevenin's theorem, find the current in resistor R_2 of $2\ \Omega$.




Solution :

1. Designate the resistor R_2 as "load".

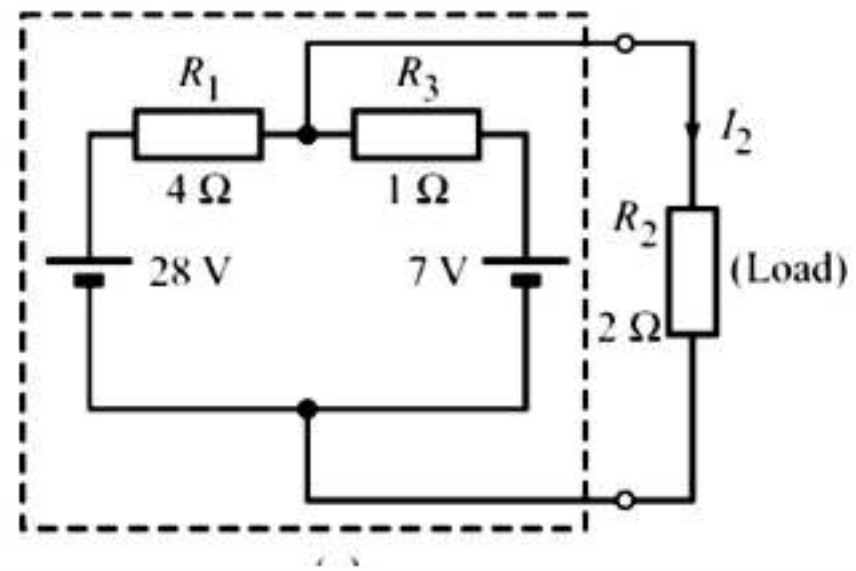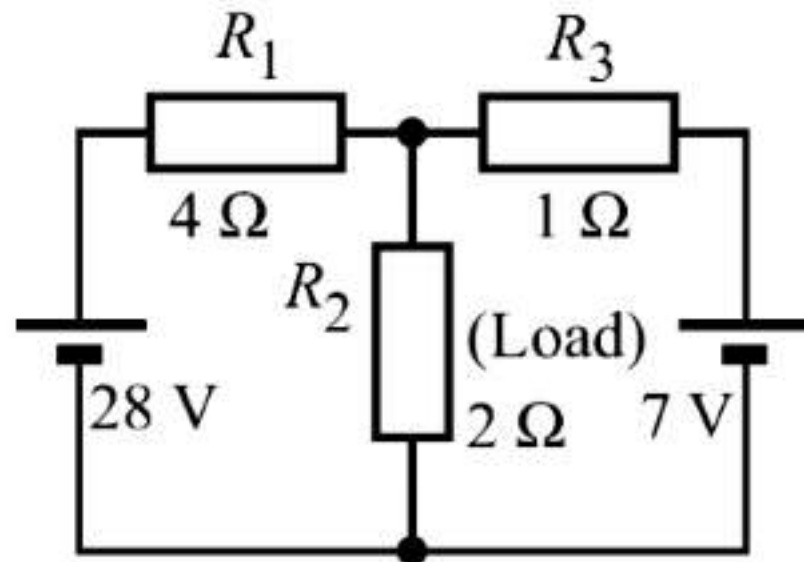

Ex: 11 Using Thevenin's theorem, find the current in resistor R_2 of $2\ \Omega$.

Calculation of V_{Th}

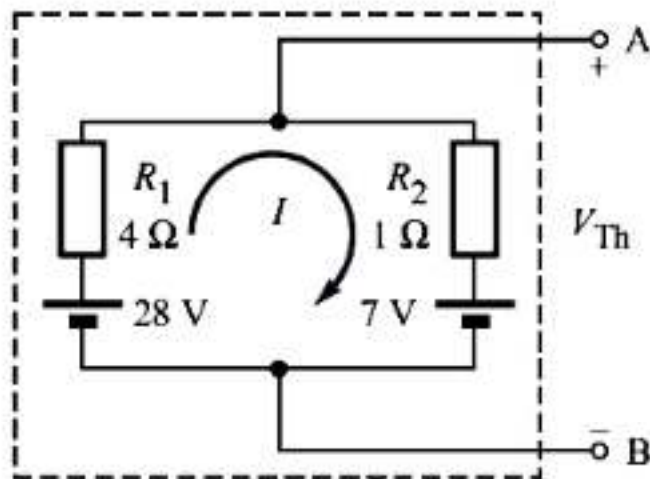


Find the *open-circuit voltage* across the terminals A-B,

$$I = \frac{28 - 7}{4 + 1} = \frac{21}{5} = 4.2\text{ A};$$

$$V_{AB} = 7 + 4.2 \times 1 = \mathbf{11.2\text{ V}}$$

Thevenin's voltage, $V_{Th} = V_{AB} = \mathbf{11.2\text{ V}}$

Calculation of R_{Th}

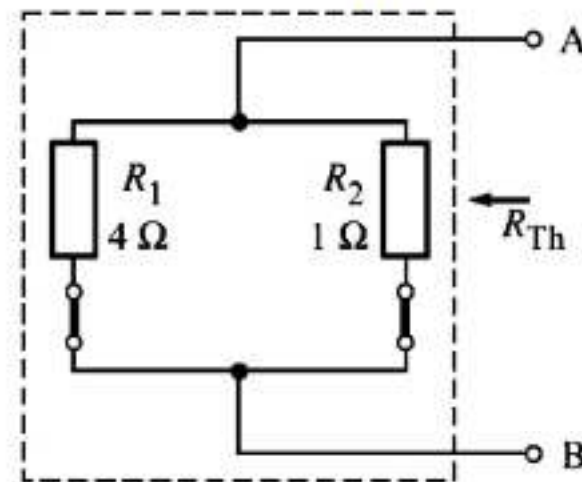


Find the resistance between terminals A and B. This is the *Thevenin's resistance*, R_{Th} . Thus,

$$R_{Th} = 1\ \Omega \parallel 4\ \Omega = \frac{1 \times 4}{1 + 4} = \mathbf{0.8\ \Omega}$$


Ex:11 Using Thevenin's theorem, find the current in resistor R_2 of $2\ \Omega$.

Thevenin's equivalent

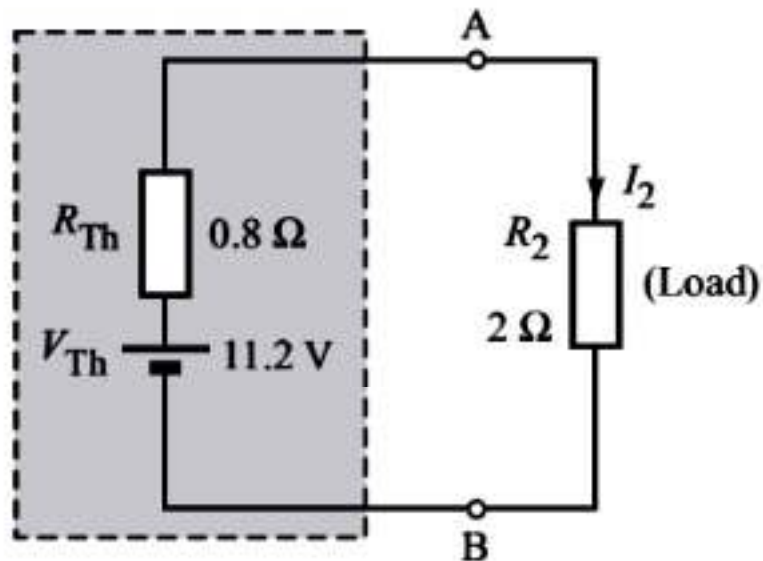


$$I_2 = \frac{V_{Th}}{R_{Th} + R_2} = \frac{11.2}{0.8 + 2} = \mathbf{4\ A}$$

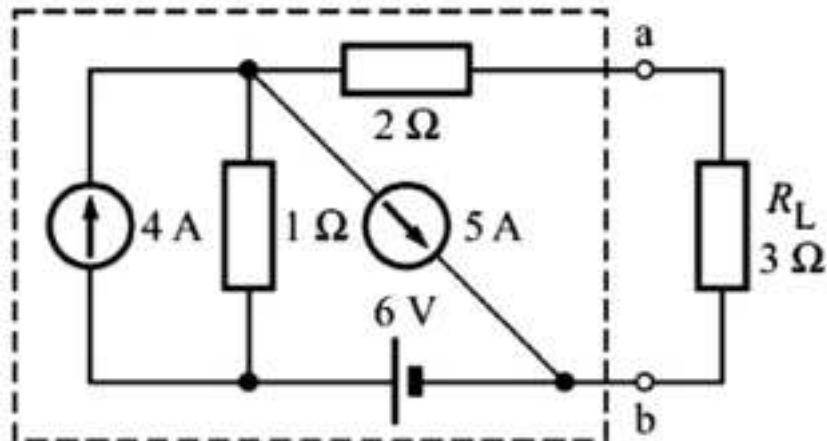Ex:12 Determine voltage across 3- Ω by applying Thevenin's theorem.




Solution : Calculation of V_{Th}

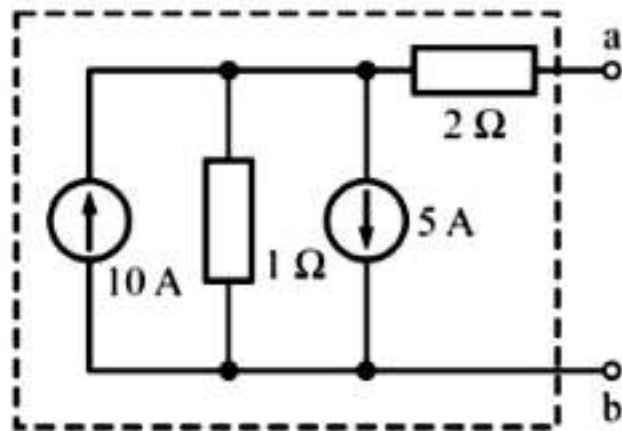- We treat the 3- Ω resistor as load.
- V_{Th} = open-circuit voltage (with R_L removed).




Use Source transformation Technique

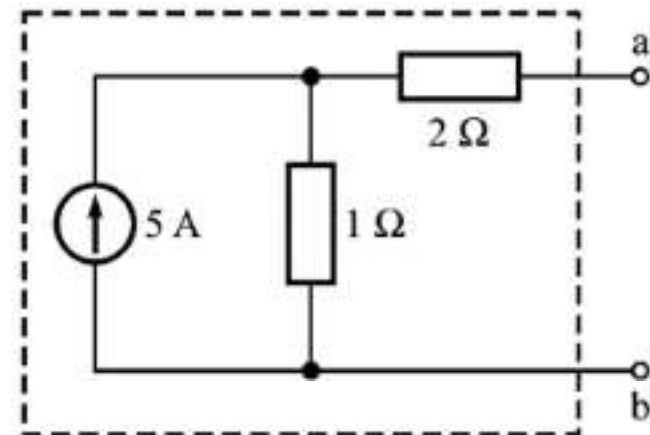


$$V_{Th} = 5 \times 1 = 5 \text{ V}$$

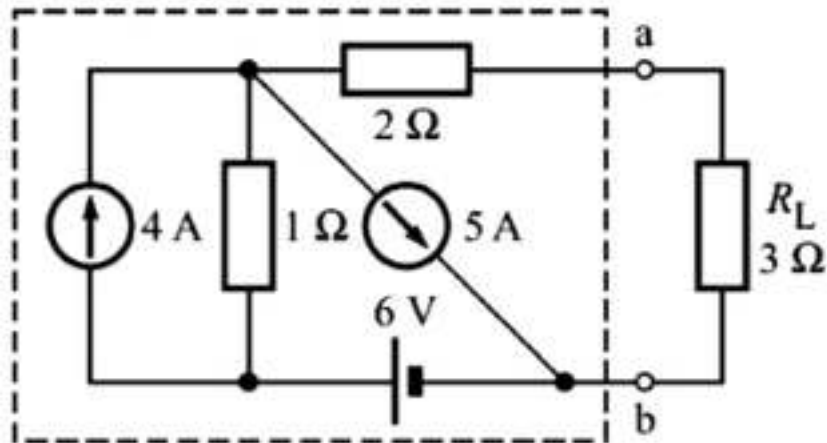Ex:12 Determine voltage across 3- Ω by applying Thevenin's theorem.




Thevenin's equivalent

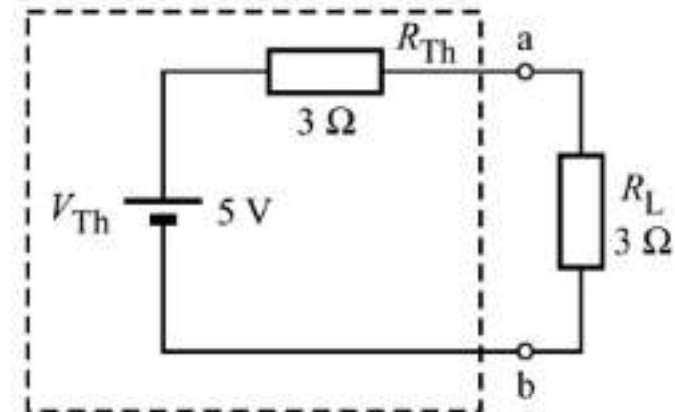

Calculation of R_{Th}

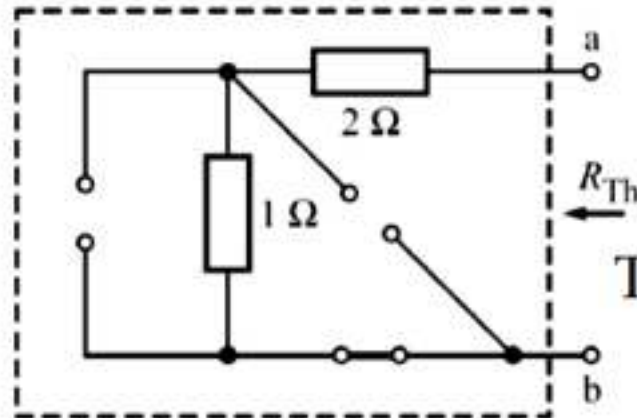turn off all the sources in the circuit within box and get the circuit




Thus, $R_{Th} = 3$

Now, apply VDR, we get

$$V_L = 5 \times \frac{3}{3+3} = 2.5 \text{ V}$$


Ex:13 Determine voltage across 2- Ω by applying Thevenin's theorem.

(a) Given circuit

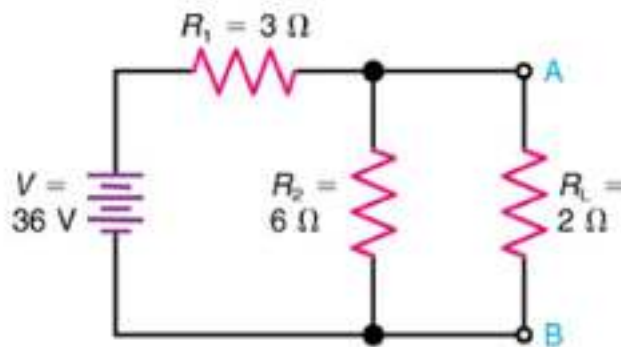


(a)

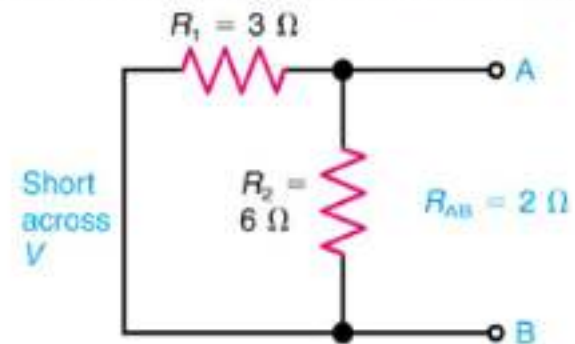(c) Short-circuit V to find that R_{AB} is 2 Ω .




(c)

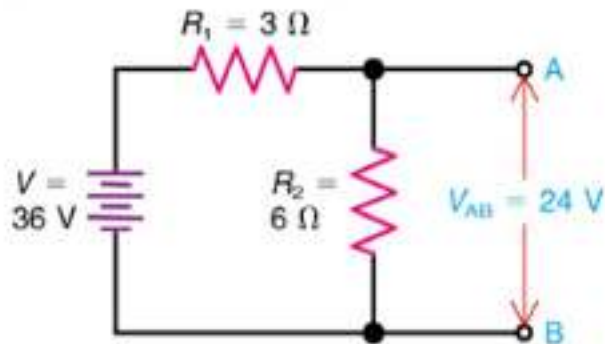(b) Disconnect R_L to find that V_{AB} is 24V.




(b)

(d) Thevenin equivalent circuit.

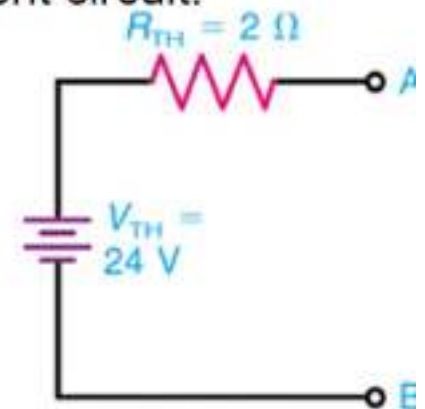

(d)

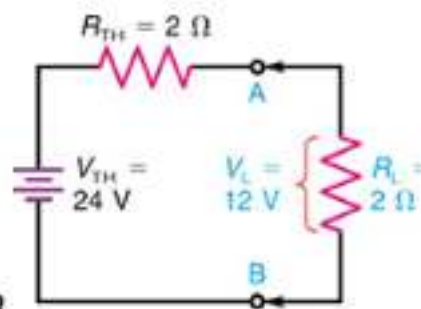
(e) Reconnect R_L at terminals A and B to find that V_L is 12V.




(e)

Ex:14 Determine voltage across 6- Ω by applying Thevenin's theorem.


(a) Given circuit

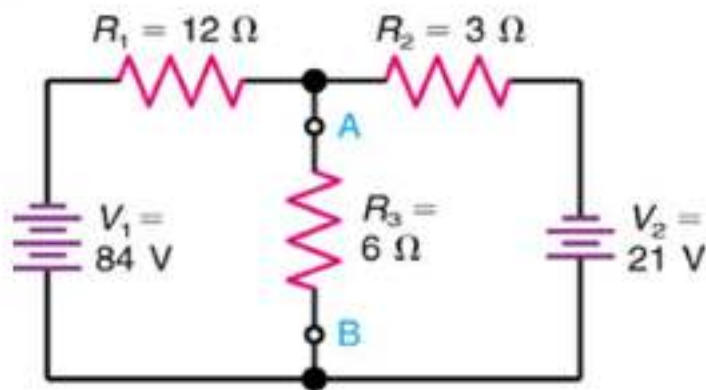

(a)

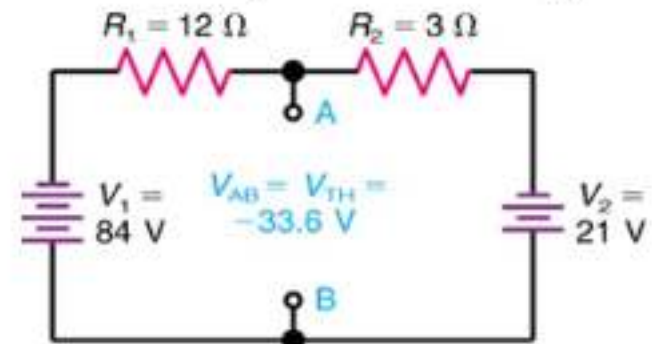
b) Disconnect R_3 to find that V_{AB} 

(b)

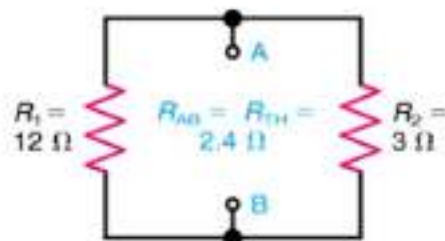(c) Short-circuit V_1 and V_2 to find that R_{AB} 

(c)


(d) Thevenin equivalent

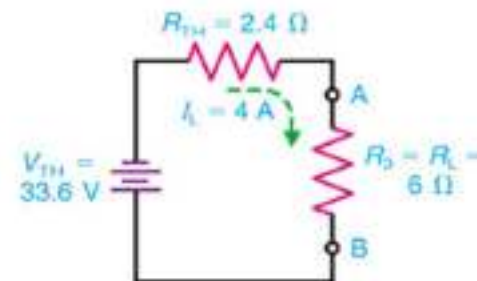

(d)


Ex:15 Find the voltage drop across R_L

(a) Given circuit

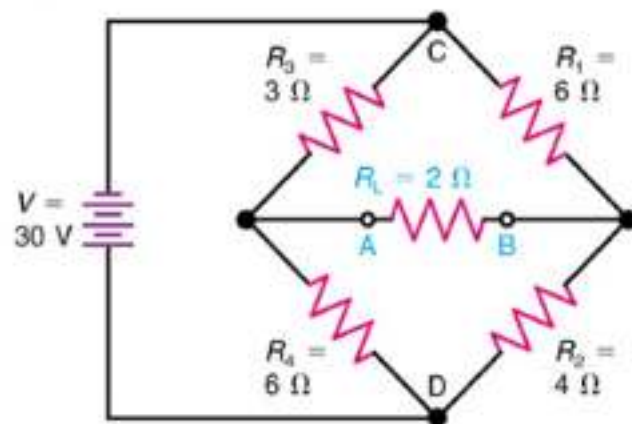


(a)

(b) Disconnect R_L to find V_{AB}

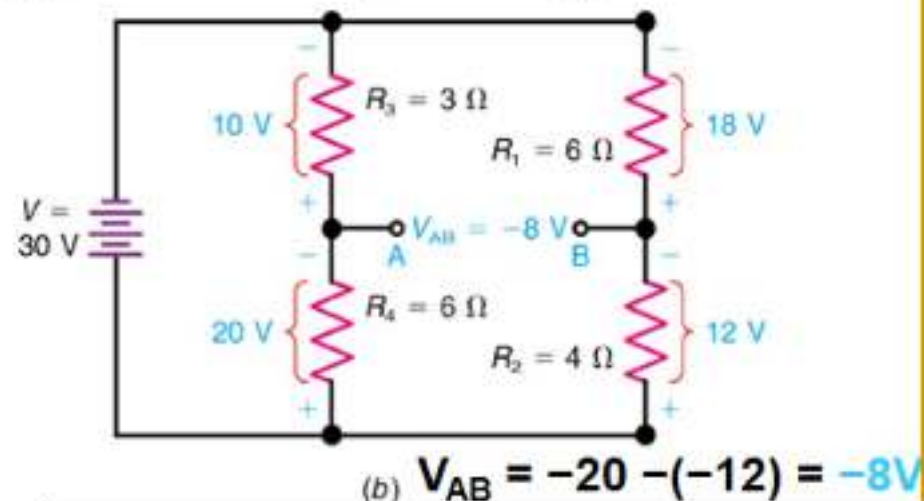


(c) With source V short-circuited

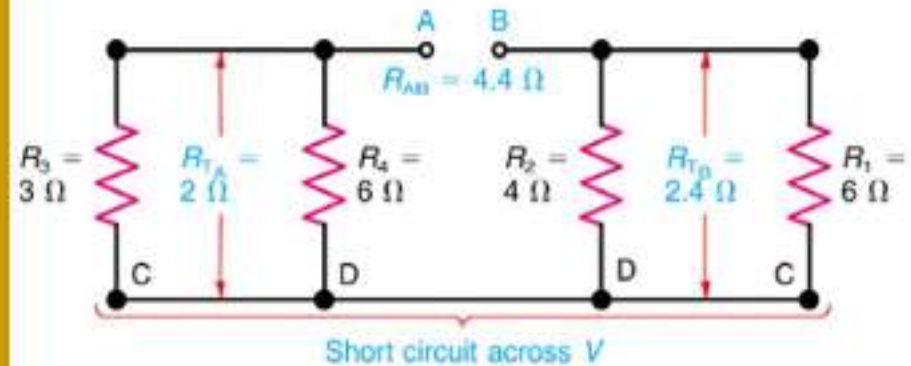


$$R_{AB} = R_{TA} + R_{TB} = 2 + 2.4 = 4.4 \Omega$$


(d) Thevenin equivalent

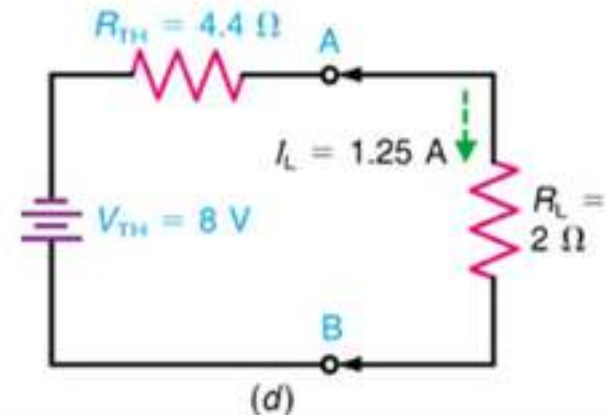

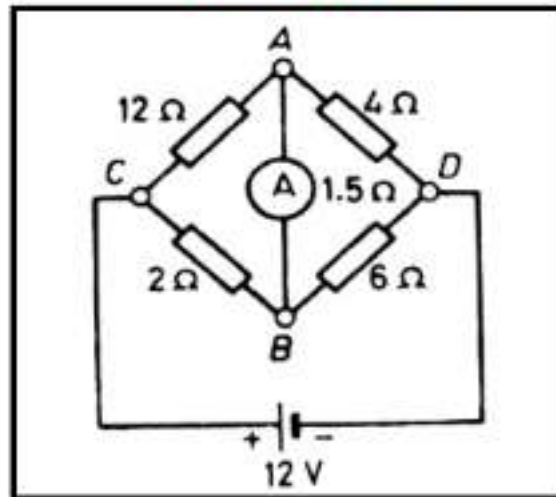Ex:16 Using Thevenin's Theorem, find current in ammeter A of resistance $1.5\ \Omega$ for the given circuit



Solution : Calculation of V_{Th}

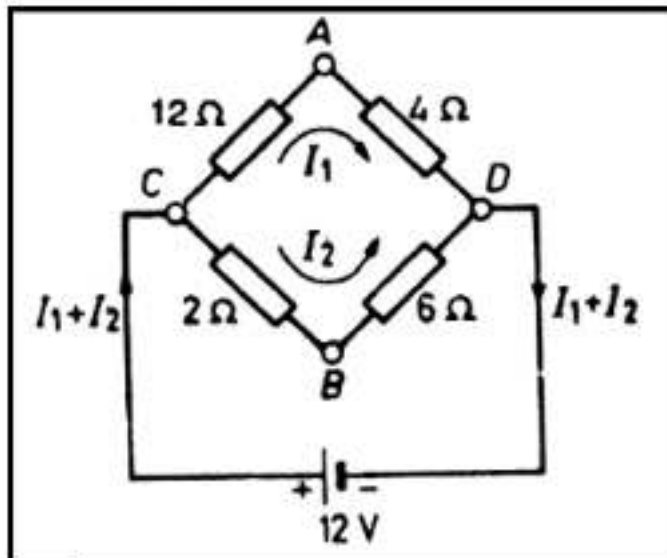



$$I_1 = \frac{12}{12+4} = 0.75\text{ A} \quad \text{and}$$

$$I_2 = \frac{12}{2+6} = 1.5\text{ A}$$


$$\begin{aligned} \therefore V_{Th} = V_{oc} = V_{AB} &= V_{AD} - V_{BD} \\ &= 0.75 \times 4 - 1.5 \times 6 = -6\text{ V} \end{aligned}$$

Calculation of R_{Th}

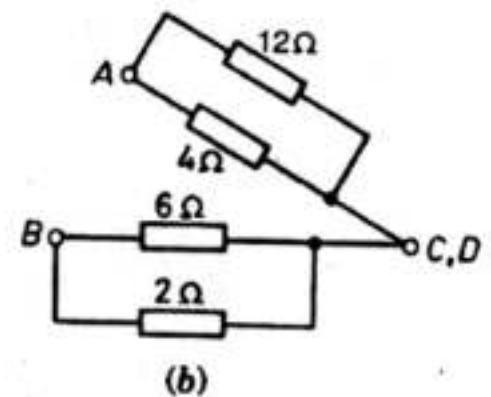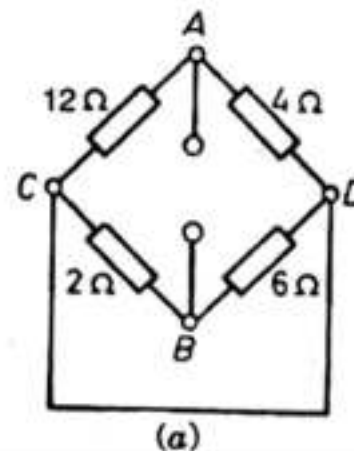Replace the voltage sources by a short-circuit, and find resistance between A and B .




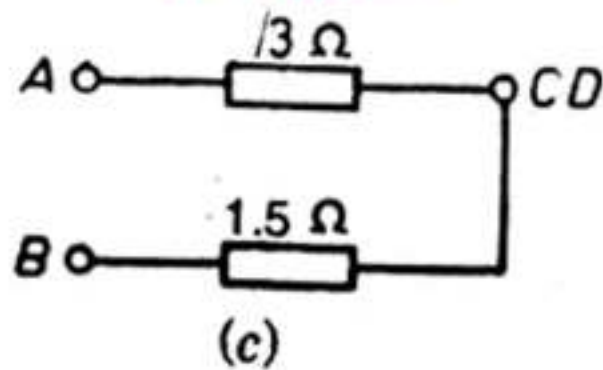Ex:16 Using Thevenin's Theorem, find current in ammeter A of resistance $1.5\ \Omega$ for the given circuit





$$\therefore I = \frac{V_{Th}}{R_{Th} + R_L} = \frac{-6}{4.5 + 1.5} = -1\text{ A}$$

Thevenin's equivalent

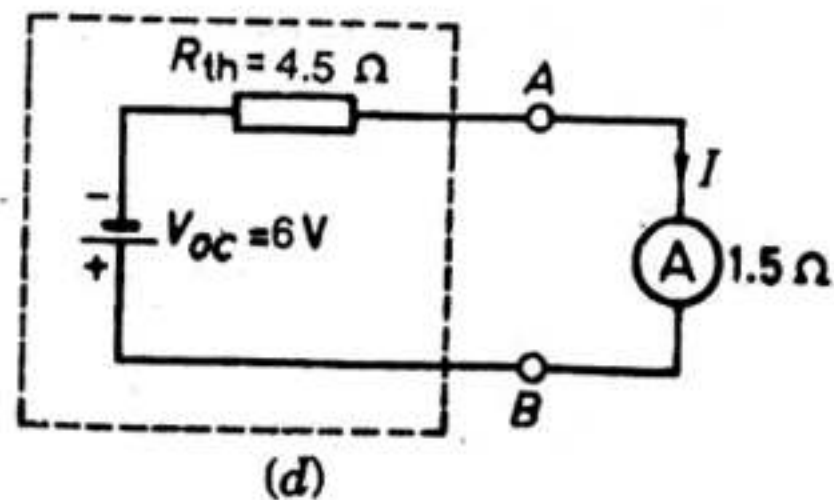

Norton's Theorem


- It is dual of Thevenin's Theorem.
- **Statement:** It states that a linear two-terminal circuit (Fig. a) composed of passive and active elements can be replaced by an equivalent circuit (Fig. b) consisting of a current source I_N in parallel with a resistor R_N ,
- Where, I_N is the short circuit current through the terminals.
 R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.

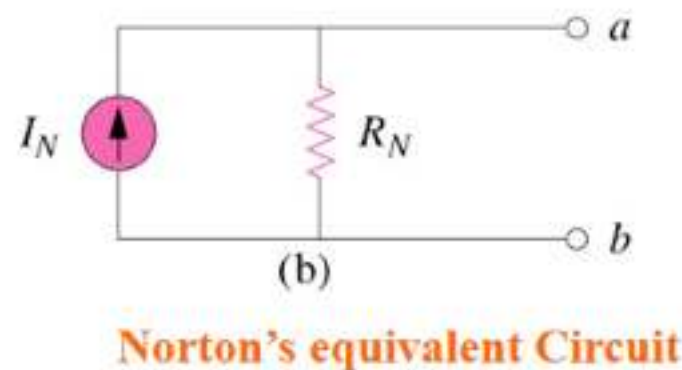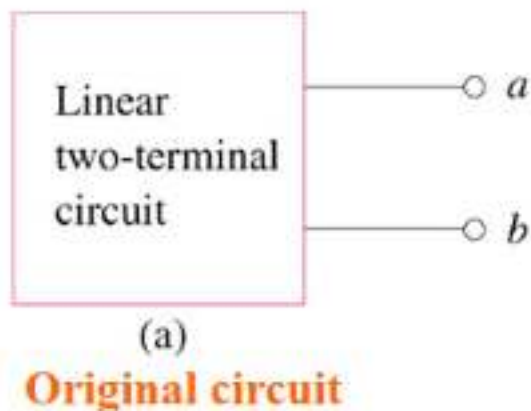

Norton's Theorem


■ Calculation of I_N

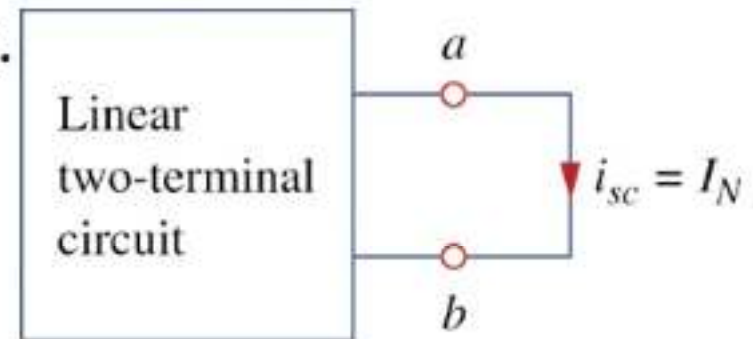The current I_N is the **short-circuit current** developed through 'ab' terminals when the load is replaced with short circuit in original network.




■ Calculation of R_N

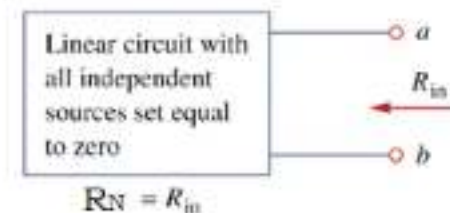The parallel resistance R_N is the equivalent resistance looking back into the network at the terminals 'ab' with **all the sources** within the network made **inactive**, or **dead** (as in Thevenin's Theorem).




Norton's Theorem

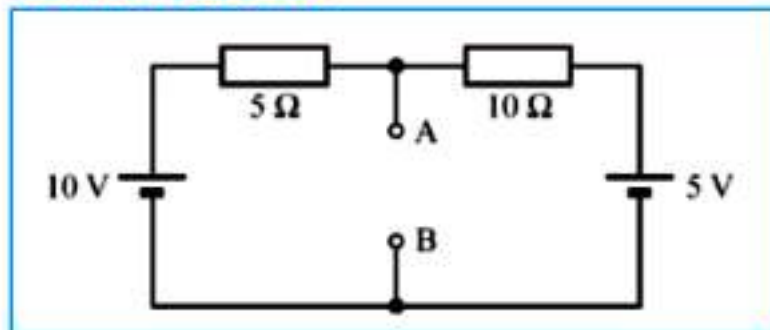Ex:1 Obtain the Norton's equivalent circuit with respect to the terminals AB for the network shown and also find current in 5Ω if connected between AB.




Solution : (i) Calculation of I_N

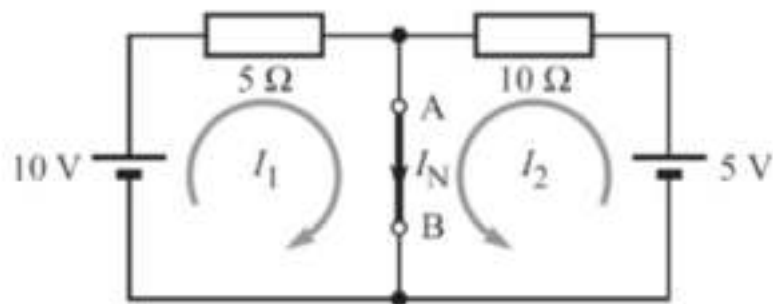


$$\therefore I_N = I_1 + I_2 = \frac{10}{5} + \frac{5}{10} = 2.5 \text{ A}$$

(ii) Calculation of R_N

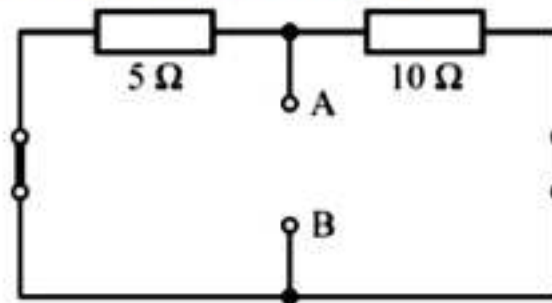

$$\therefore R_N = \frac{5 \times 10}{5 + 10} = \frac{10}{3} \Omega$$


(iii) Norton's equivalent circuit

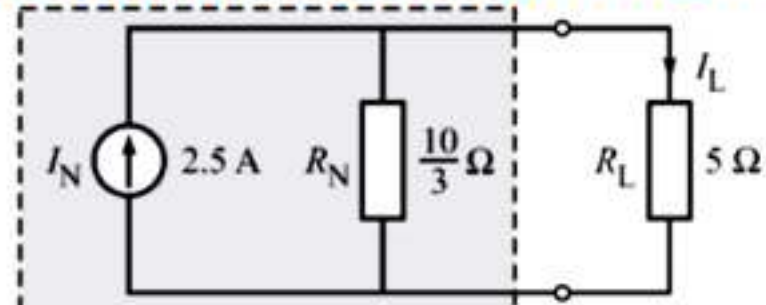


$$I_L = I_N \frac{R_N}{R_N + R_L} = 2.5 \times \frac{(10/3)}{(10/3) + 5} = 1 \text{ A}$$

Norton's Theorem

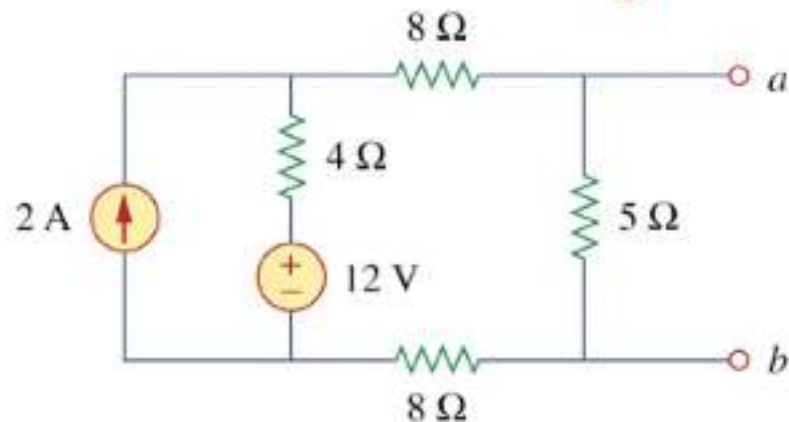Ex:2 Find the Norton equivalent circuit of the circuit in Fig



Solution : (i) Calculation of I_N

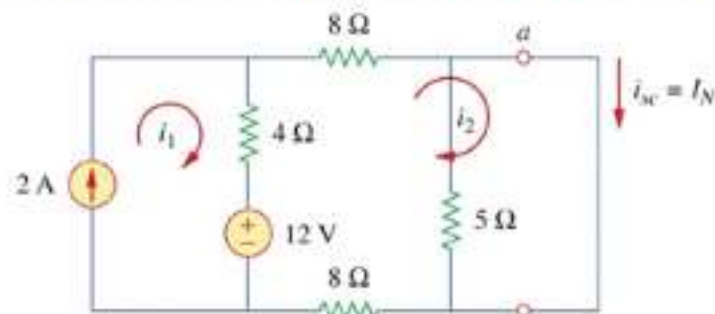


short-circuit terminals a and b .

$$\text{Mesh : } i_1 = 2\text{A}, \quad 20i_2 - 4i_1 - i_2 = 0$$

$$i_2 = 1\text{A} = i_{sc} = I_N$$

(ii) Calculation of R_N

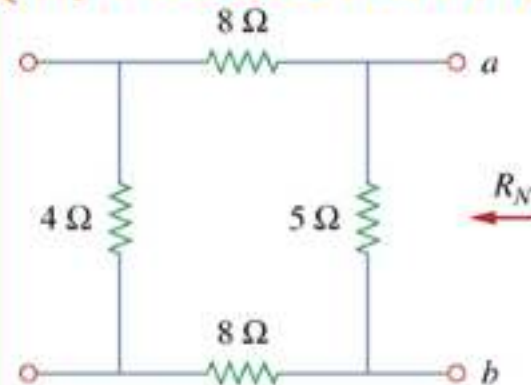


$$R_N = 5 \parallel (8 + 4 + 8)$$

$$= 5 \parallel 20 = \frac{20 \times 5}{25} = 4\Omega$$

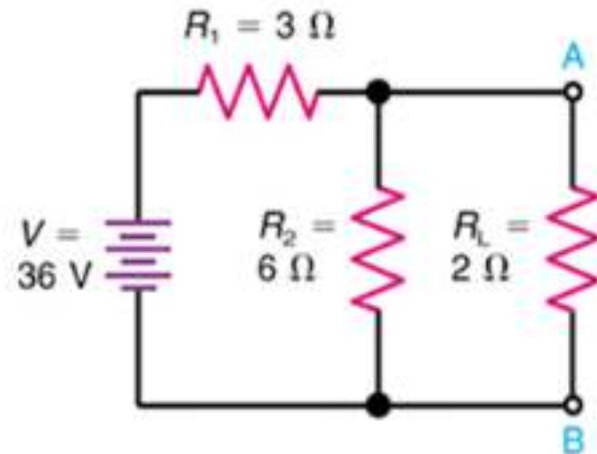
(iii) Norton's equivalent circuit

Norton's Theorem


Ex:3 Find current in $2\ \Omega$ using Norton theorem





Solution : (i) Calculation of I_N

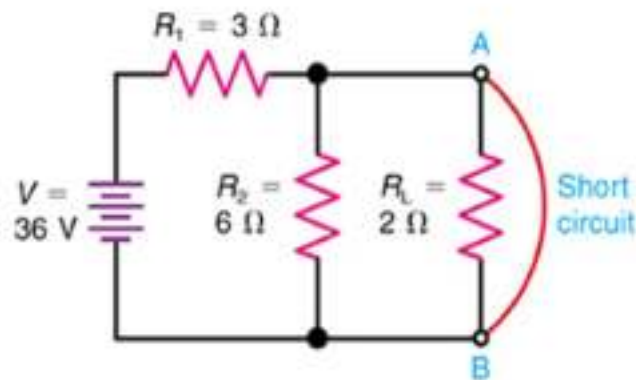

(ii) Calculation of R_N

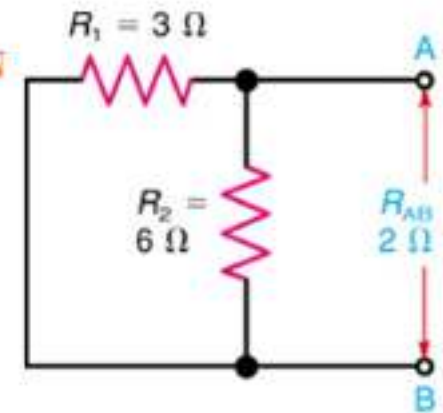


(iii) Norton's equivalent circuit

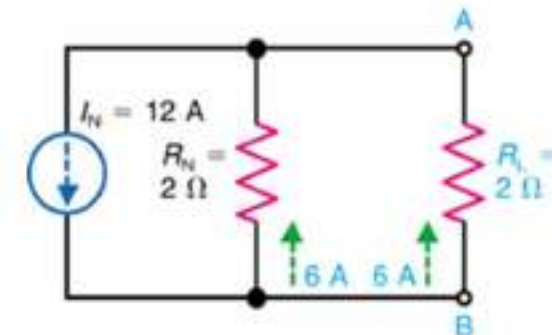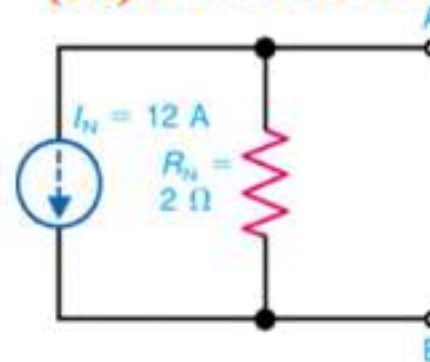


$$I_L = I_N \times \frac{R_N}{R_N + R_L} = 12 \times \frac{2}{2 + 2} = 6\text{ A}$$

Norton's Theorem

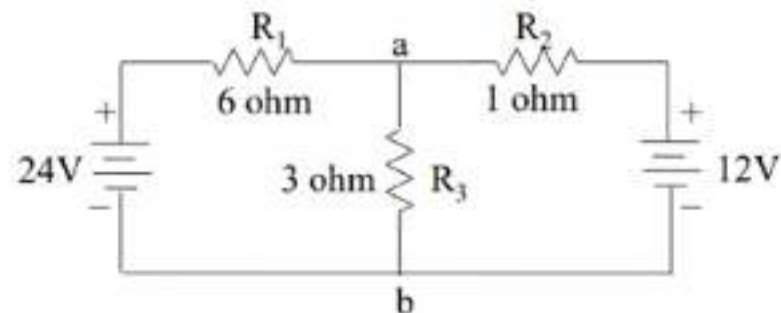Ex:4 Find the current through $3\ \Omega$ by Norton's Theorem




Solution : (i) Calculation of I_N

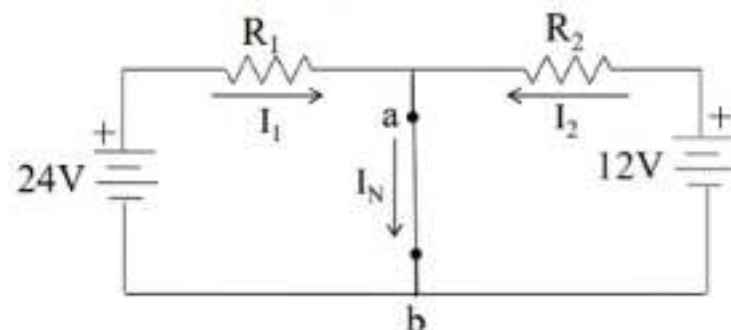



$$I_N = I_1 + I_2 = \frac{24}{6} + \frac{12}{1} = 16\text{A}$$

(ii) Calculation of R_N

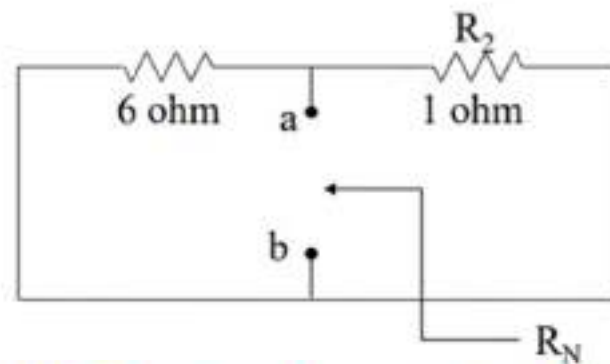


$$R_N = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 1}{6 + 1} = 0.857\ \Omega$$

(iii) Norton's equivalent circuit

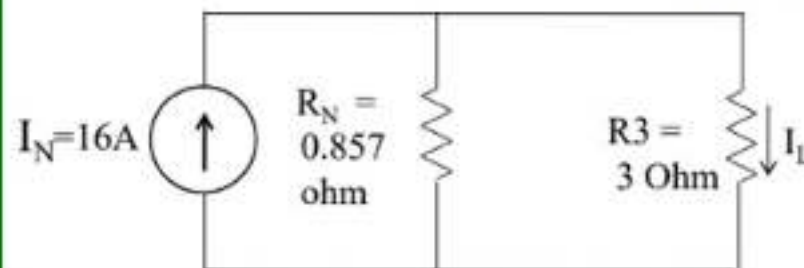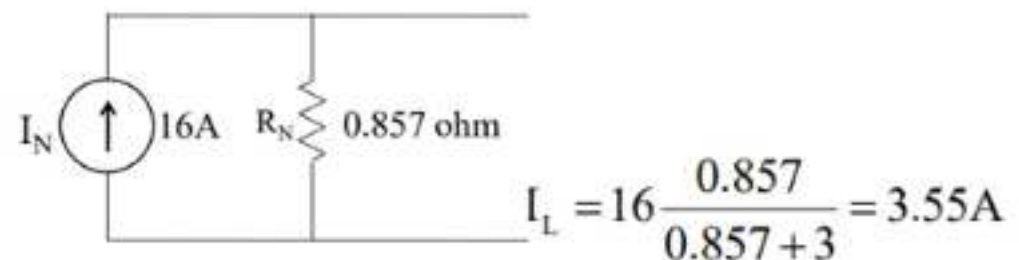


Norton's Theorem

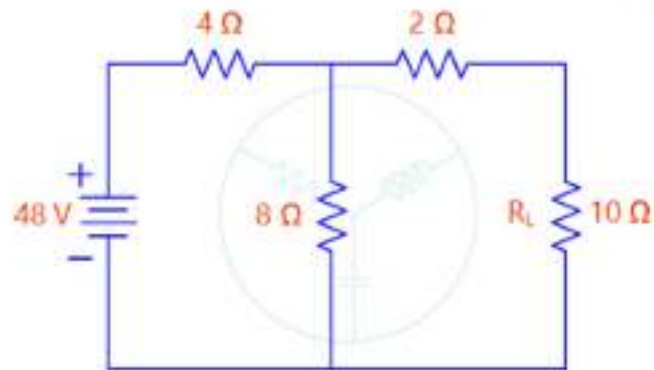Ex:5 Find the current through $10\ \Omega$ by Norton's Theorem



Solution : (i) Calculation of I_N

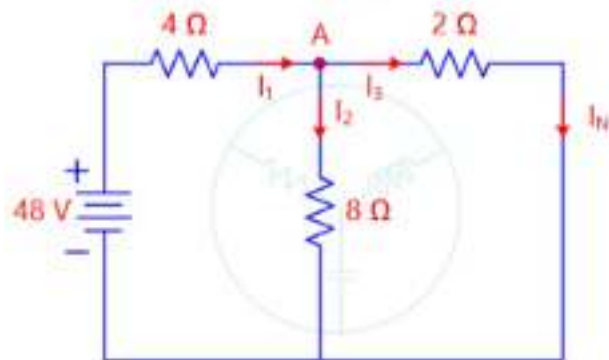


$$R_{eq} = 4 + \frac{8 \times 2}{8 + 2} = 5.6\ \Omega$$


$$I_1 = \frac{V}{R_{eq}} = \frac{48}{5.6} = 8.57\text{ A}$$

$$I_N = I_3 = 8.57 \times \frac{8}{8 + 2} = 6.86\text{ A}$$

(ii) Calculation of R_N

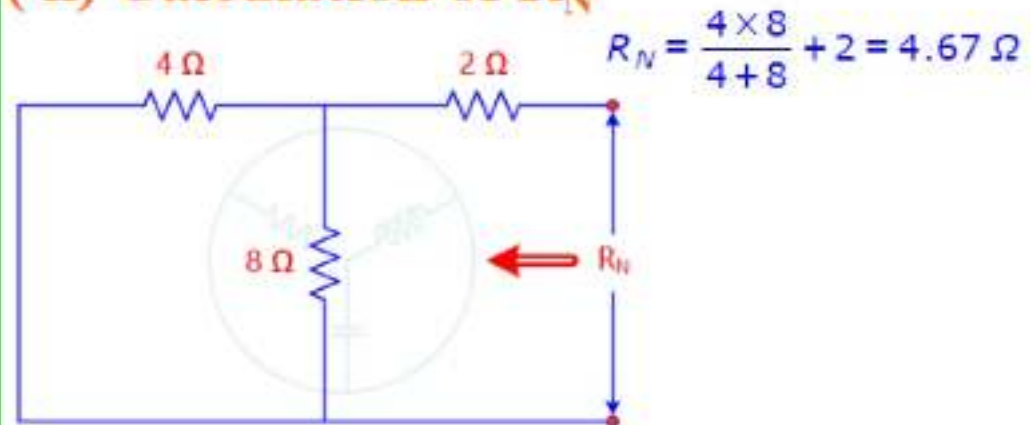


(iii) Norton's equivalent circuit

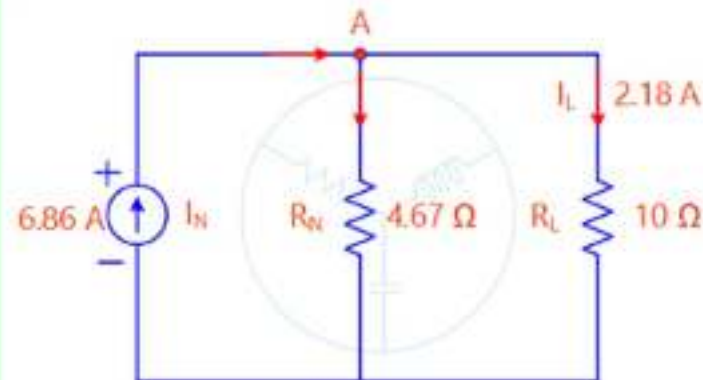


$$I_L = I_N \times \frac{R_N}{R_N + R_L} = 6.86 \times \frac{4.67}{4.67 + 10} = 2.18\text{ A}$$

Norton's Theorem

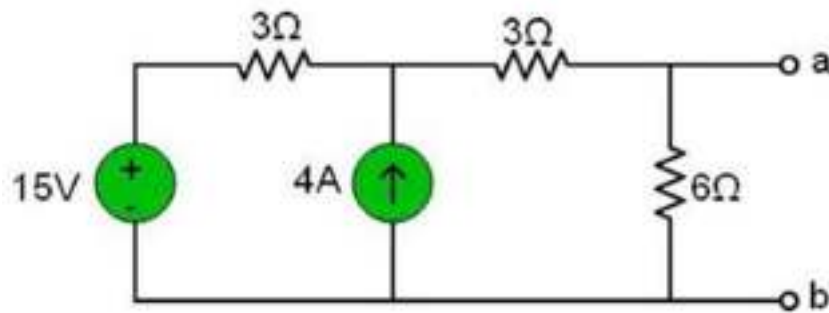Ex:6 Find Norton equivalent circuit across 'ab'




(ii) Calculation of R_N

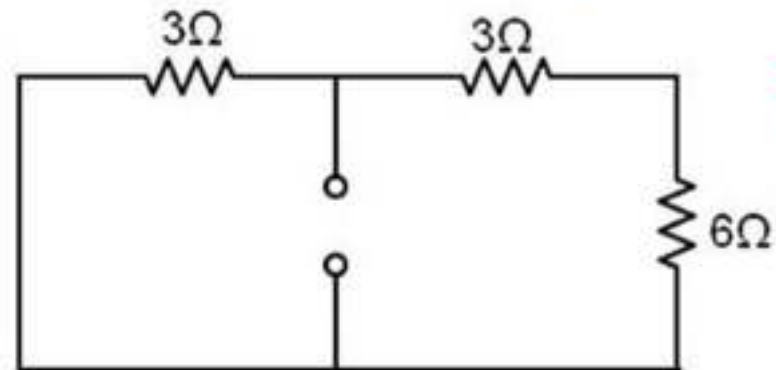


$$R_N = 3\Omega$$

Solution : (i) Calculation of I_N

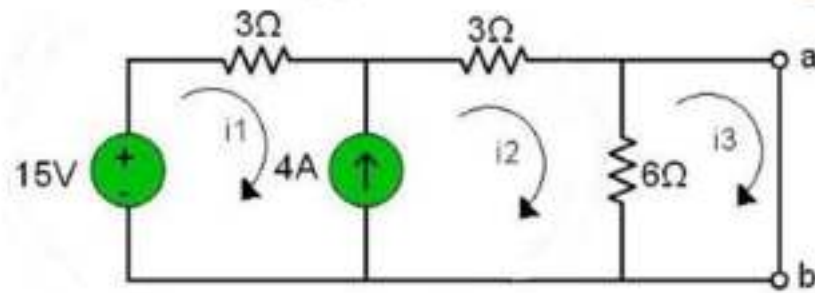


$$I_N = 4.5A$$

(iii) Norton's equivalent circuit

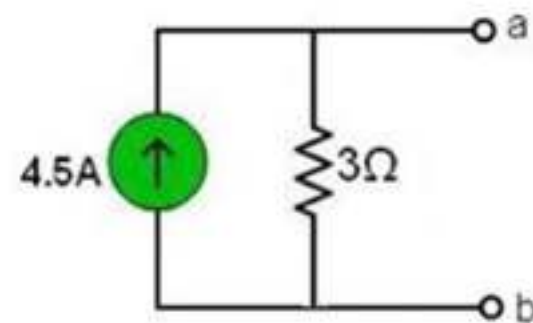


Norton's Theorem

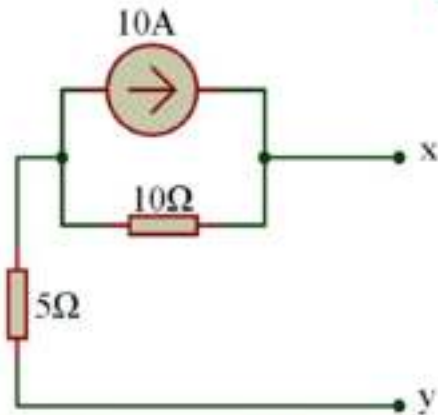Ex:7 Find Norton equivalent circuit across 'XY'




Solution : (i) Calculation of I_N

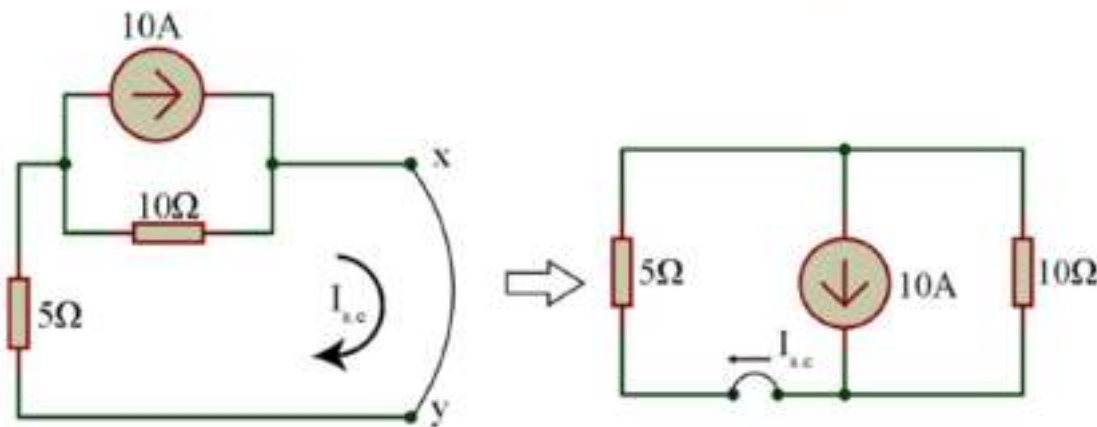

Here, $I_{s.c}$ is the current through 5Ω resistor.


$$\therefore I_{s.c} = 10 \times \frac{10}{10 + 5} = 6.67A$$

(ii) Calculation of R_N

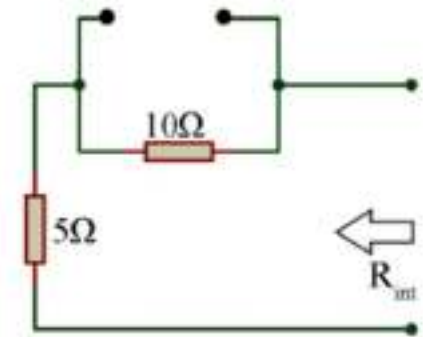

$$= 10 + 5 = 15\Omega$$


(iii) Norton's equivalent circuit

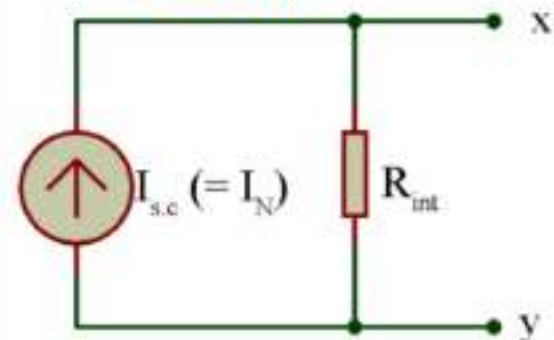


$$I_N = 6.67A; R_{int} = 15\Omega.$$

Norton's Theorem

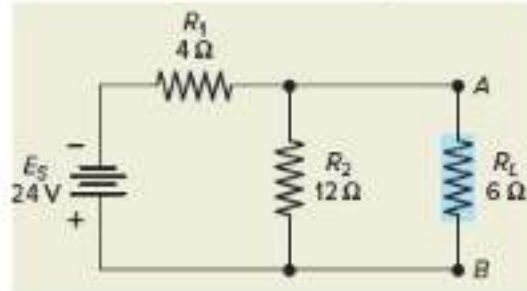Ex:8 Find current flowing in the 6Ω and also find current through 3Ω if 6Ω is replaced by 3Ω Norton theorem (ii) Calculation of R_N




Solution : (i) Calculation of I_N

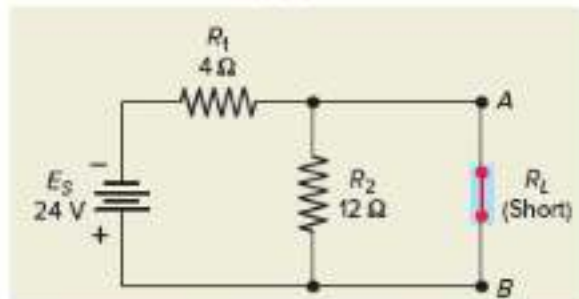

$$I_N = \frac{E_S}{R_1}$$

$$= \frac{24 \text{ V}}{4 \Omega}$$

$$= 6 \text{ A}$$

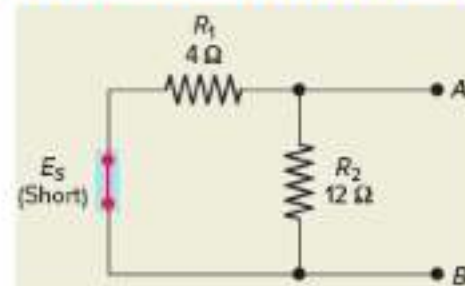


$$R_N = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$= \frac{4 \Omega \times 12 \Omega}{4 \Omega + 12 \Omega}$$

$$= 3 \Omega$$

(iii) Norton's equivalent circuit

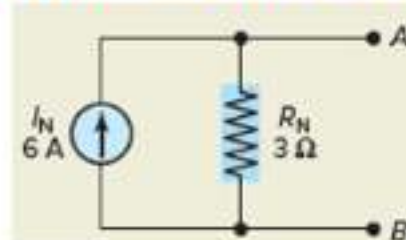

$$I_{R_L} = \frac{R_N}{R_N + R_L} \times I_N$$


$$= \frac{3 \Omega}{3 \Omega + 6 \Omega} \times 6 \text{ A}$$

$$= 2 \text{ A}$$

$$E_{R_L} = I_{R_L} \times R_L$$

$$= 2 \text{ A} \times 6 \Omega$$

$$= 12 \text{ V}$$

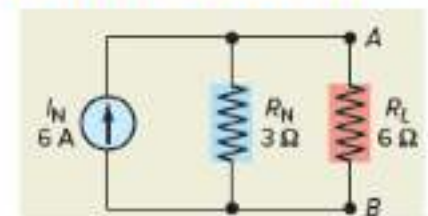

$$I_{R_L} = \frac{R_N}{R_N + R_L} \times I_N$$

$$= \frac{3 \Omega}{3 \Omega + 3 \Omega} \times 6 \text{ A}$$

$$= 3 \text{ A}$$


$$E_{R_L} = I_{R_L} \times R_L$$

$$= 3 \text{ A} \times 3 \Omega$$

$$= 9 \text{ V}$$

Norton's Theorem

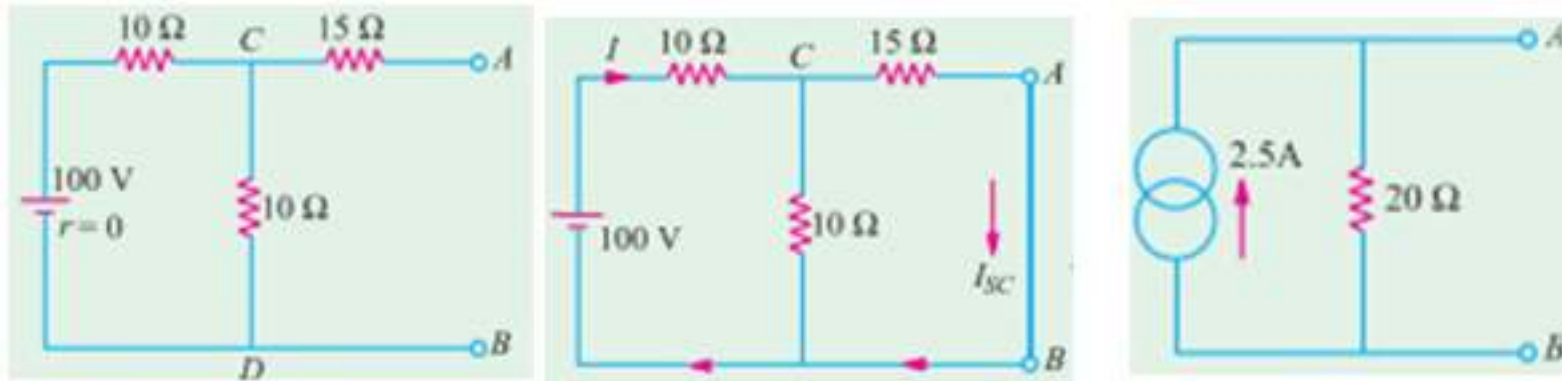Ex:9 Find Norton equivalent circuit across 'ab'



Ex:10 Find Current through $5\ \Omega$ Norton theorem

